

INTRANEX

INTRANEX is a **programmable interconnect network** that accepts a N bit input W and produces a N bit output Z. The interconnect can be programmed to realize any mapping from W to Z.

University of Cincinnati - EECE6080
FALL 2013

Max Thrun
973 919 6593
max.thrun@gmail.com
(Coordinator)

Xiaohu Qi
513 652 2075
qixiaohuihaha@gmail.com

Contents

1	Progress Report 1	8
1.1	Pinout Diagram	9
1.2	Chip Functionality	11
1.2.1	Configuring the Programmable Interconnect Network	11
1.2.2	Loading and reading a value	11
1.2.3	Test Mode	12
1.3	Design Decisions	12
1.4	Block Diagrams	13
1.4.1	Top Level	13
1.4.2	Top Level With Test Mode	13
1.4.3	Top Level Bit Sliced	14
1.4.4	Parallel Load Shift Register	15
1.4.5	Programmable Interconnect Network	16
1.5	VHDL Models	17
1.5.1	Top Level	17
1.5.2	PIN	18
1.5.3	PIN Slice	19
1.5.4	Shifter	20
1.5.5	Shifter Slice	21
1.5.6	Gates	22
1.6	VHDL Test Benches	23
1.6.1	Top Level Functional	23
1.6.2	Top Level Test Mode	25
1.6.3	PIN Slice	26
1.6.4	Shifter Slice	27
1.7	VHDL Test Bench Results	28
1.7.1	Top Level Functional	28
1.7.2	Top Level Test Mode	28
1.8	Work Division	28

2	Progress Report 2	29
2.1	Slice Layouts	30
2.1.1	PIN Slice Layout	30
2.1.2	Shift Slice Layout	31
2.2	Slice IRSIM Results	32
2.2.1	PIN Slice IRSIM Results	32
2.2.2	Shift Slice IRSIM Results	34
2.3	Slice Spice Results	36
2.3.1	PIN Slice Spice Results	36
2.3.2	Shift Slice Spice Results	38
2.4	Gate Spice Results	40
2.4.1	DFFPOSX1 Spice Results	40
2.4.2	AOI21X1 Spice Results	41
2.4.3	MUX2X1 Spice Results	42
2.4.4	INVX1 Spice Results	43
2.4.5	Leaf Component Delay Summary	43
2.5	VHDL Models With Timing	44
2.6	VHDL Testbench Results With Timing	45
2.6.1	VHDL Slice Testbench With Delays Waveform	45
2.6.2	VHDL Top Level Testbench With Delays Waveform	45
2.7	Final Simulation Comparision	46
2.8	Floor Plan	47
2.9	Major Design Decisions	48
2.10	Work Division	48

List of Figures

1.1	Pinout Diagram	9
1.2	PIN Configuration	11
1.3	Loading a value	11
1.4	Loading a value and reading the result	11
1.5	Enabling test mode and loading all DFFs	12
1.6	3 INTRANEX Chain	12
1.7	Top Level Block Diagram (3-Bit Configuration)	13
1.8	Top Level Block Diagram Showing Test Mode Logic (3-Bit Configuration)	13
1.9	Top Level Bit Sliced Block Diagram (3-Bit Configuration)	14
1.10	Parallel Load Bit-Sliced Shifter Register (3-Bit Configuration)	15
1.11	Parallel Load Shifter Register Bit-Slice	15
1.12	Bit-Sliced Programmable Interconnect Network (3-Bit Configuration)	16
1.13	Programmable Interconnect Network Bit-Slice	16
1.14	Top Level Generated RTL Diagram	17
1.15	Pin Generated RTL Diagram	18
1.16	Pin Slice Generated RTL Diagram	19
1.17	Shifter Generated RTL Diagram	20
1.18	Shifter Slice Generated RTL Diagram	21
1.19	Top Level Functional Test Bench Waveform	28
1.20	Top Level Test Mode Test Bench Waveform	28
2.1	PIN Slice Layout	30
2.2	PIN Slice Layout Internal	30
2.3	PIN Slice Layout	31
2.4	PIN Slice Layout Internal	31
2.5	PIN Slice IRSIM Functional Results	32
2.6	PIN Slice Critical Path	33
2.7	PIN Slice IRSIM Critical Path Delay	33
2.8	Shift Slice IRSIM Functional Results	34
2.9	Shift Slice Critical Path	35

2.10 Shift Slice IRSIM Critical Path Delay	35
2.11 PIN Slice Spice Functional Results	36
2.12 PIN Slice Spice Critical Path Delay	37
2.13 Shift Slice Spice Functional Results	38
2.14 Shift Slice Spice Critical Path Delay	39
2.15 DFFPOSX1 Spice Results	40
2.16 AOI21X1 Spice Results	41
2.17 MUX2X1 Spice Results	42
2.18 INVX1 Spice Results	43
2.19 VHDL PIN Slice With Delays Waveform	45
2.20 VHDL Shift Slice With Delays Waveform	45
2.21 VHDL Top Level Functional Test Bench With Delays Waveform	45
2.22 VHDL Top Level Test Mode Test Bench With Delays Waveform	45
2.23 Floor Plan Diagram	47

List of Tables

1.1	Pin Descriptions	10
1.2	Task Assignment	28
2.1	PIN Slice IRSIM Critical Path Delays	33
2.2	Shift Slice IRSIM Critical Path Delays	35
2.3	PIN Slice Spice Critical Path Delays	37
2.4	Shift Slice Spice Critical Path Delays	39
2.5	DFFPOSX1 Delays	40
2.6	AOI21X1 Delays	41
2.7	MUX2X1 Delays	42
2.8	INVX1 Delays	43
2.9	Worst Case Delay Summary	43
2.10	Critical Path Delay Comparison	46
2.11	Task Assignment	48

Listings

1.1	Top Level VHDL Module	17
1.2	PIN VHDL Module	18
1.3	PIN Slice VHDL Module	19
1.4	Parallel Load Shifter VHDL Module	20
1.5	Parallel Load Shifter Slice VHDL Module	21
1.6	AOI21X1 VHDL Module	22
1.7	DFFPOSX1 VHDL Module	22
1.8	INVX1 VHDL Module	22
1.9	MUX2X1 VHDL Module	22
1.10	Top Level VHDL Test Bench	23
1.11	Python Vector Generator	24
1.12	Top Level Test Mode VHDL Test Bench	25
1.13	PIN Slice VHDL Test Bench	26
1.14	Parallel Load Shifter Slice VHDL Test Bench	27
2.1	Python PIN Slice IRSIM CMD File Generator	32
2.2	Python Shift Slice IRSIM CMD File Generator	34
2.3	Python PIN Slice Spice File Generator	36
2.4	Python Shift Slice Spice File Generator	38
2.5	Python DFFPOSX1 Spice File Generator	40
2.6	Python AOI21X1 Spice File Generator	41
2.7	Python MUX2X1 Spice File Generator	42
2.8	Python INVX1 Spice File Generator	43
2.9	AOI21X1 VHDL Module With Delay	44
2.10	DFFPOSX1 VHDL Module With Delay	44
2.11	INVX1 VHDL Module With Delay	44
2.12	MUX2X1 VHDL Module With Delay	44

Chapter 1

Progress Report 1

1.1 Pinout Diagram

The pinout diagram for INTRANEX is shown below in Figure 1.1. Pins that are currently unutilized will be assigned to various internal logic signals once the floorplan is finalized. Note the symmetry of the core functionality. This was done so that multiple INTRANEX chip can be directly chained together with minimal routing effort during PCB layout.

 


Figure 1.1: Pinout Diagram

The table below shows each pin and its corresponding name, type, and a brief description of its functionality. Type is of either I (Input), O (Output), or P (Power).

Pin #	Name	Type	Description
1	–	-	–
2	–	-	–
3	–	-	–
4	–	-	–
5	PSI	I	PIN serial input
6	PCLKI	I	PIN clock input
7	TESTI	I	Test Mode enable input
8	SI	I	Serial input
9	SCLKI	I	Serial clock input
10	LDI	I	Parallel load input
11	TII	I	Test inverter input
12	TIO	O	Test interter output
13	TFD	I	Test flip-flop D input
14	TFC	I	Test flip-flop clock input
15	TFQ	O	Test flop-flop Q output
16	GND	P	–
17	–	-	–
18	–	-	–
19	–	-	–
20	–	-	–
21	LDO	O	Parallel load output
22	SCLKO	O	Serial clock output
23	SO	O	Serial output
24	TESTO	O	Test Mode enable output
25	PCLKO	O	PIN clock output
26	PSO	O	PIN serial output
27	–	-	–
28	–	-	–
29	–	-	–
30	TSI	I	Test shift slice serial input
31	TSO	O	Test shift slice serial output
32	TSCI	I	Test shift slice clock input
33	TSCO	O	Test shift slice clock output
34	TSLI	I	Test shift slice load input
35	TSLO	O	Test shift slice load output
36	VDD	P	–
37	TPI	I	Test pin slice serial input
38	TPO	O	Test pin slice serial output
39	TPCI	I	Test pin slice clock input
40	TPCO	O	Test pin slice clock output

Table 1.1: Pin Descriptions

1.2 Chip Functionality

The major function of this chip is to take an N bit input and translate any bit position to any other position. This allows for commonly desired functionality such as bit reversing or nibble swapping. To accomplish this we use a N by N bit interconnect network known as the PIN (Programmable Interconnect Network). The PIN is configured to perform the desired bit mappings by clocking in the mappings using the PSI (PIN Shift Input) and PCLKI (PIN Clock Input) pins. The value to be manipulated, called the Input Value, Shift Value or Shifter Value, is then clocked in serially using the SI (Shifter Input) and SCLKI (Shifter Clock Input) pins. To obtain the result the LDI (Load Input) pin is pulled high and the SCLKI pin is pulsed to latch the result in to the shift register. Once the result is latched the LDI pin is de-asserted and the result can be clocked out of the SO (Shifter Output) pin. Note that the input value is clocked in MSB first and the output value is clocked out MSB first as well.

1.2.1 Configuring the Programmable Interconnect Network

A timing diagram illustrating the PIN configuration process for a 3-Bit INTRANEX is shown below. For a 3-Bit input value a 3x3 grid is required resulting in a PIN configuration vector of 9 Bits. The mapping for each of these bits is also labeled and will be explained further in later sections.

 


Figure 1.2: PIN Configuration

1.2.2 Loading and reading a value

Loading an input value is achieved by clocking the value in on the SI pin using the SCLKI pin. The LDI pin must be held low during this operation. The diagram below illustrates this process and shows the bit definitions of the value being clocked in.

 


Figure 1.3: Loading a value

After the value has been loaded in the result is clocked out in a similar fashion. To first latch the result the LDI pin needs to be held high and the SCLKI pin pulsed. The MSB of the result is now available on the SO pin. The LDI pin should now be held low while clocking out the remaining result bits.

 


Figure 1.4: Loading a value and reading the result

1.2.3 Test Mode

Test Mode is enabled by pulling the **TESTI** pin high. When this occurs the output of the internal input value shift register is rerouted to connect to the input of the PIN network bypassing its normal **PSI** input. Additionally the **SCLK0** signal is also routed to the PIN bypassing its normal **PCLKI** signal. Finally the **PS0** signal is routed to the **S0** pin. This allows values that are clocked in via the **SI** pin to propagate through the shifter and then through the PIN and then out the **S0** pin. The fact that the values come out the **S0** pin allows multiple INTRANEX chips to be directly chained and tested in circuit using only the **SI** and **SCLKI** pins of the first chip in the chain. Note that the **LDI** pin must be held low during this entire operation in order to ensure proper shifting through the input value shift register.

 


Figure 1.5: Enabling test mode and loading all DFFs

1.3 Design Decisions

When evaluating design concepts and possible solutions we prioritized a few key factors that we wanted to achieve. The first is a fully bit-sliced solution where each slice can directly connect to the next with minimal wiring overhead and zero additional logic. This will allow us to utilize Magics `Array` functionality to quickly build up our chip and allow us to easily scale to any desired size. As we see in later sections we were able to achieve a fully bit-sliced design with zero logic overhead.

In order to achieve totally minimized wiring overhead it would be necessary to design two different slice layouts, one of which is mirrored and flipped. This would allow each slice row in the PIN to share a power rail with the rows above and below it and also minimize the length of the row-to-row wiring. This design however greatly increases the complexity of the VHDL design as wiring the rows together becomes trickier. Additionally we would have to maintain two different versions of the PIN slices. We decided to instead go with a design where all slices are exactly identical and the interconnect between them is linear. This allows for easier calculation of PIN configuration values as every row has the same index order. The only real disadvantage to this design is that we will require long interconnects between slices. We are assuming for now that even with the added capacitance of these long interconnects we will still be able to achieve max clock speeds of greater than 50Mhz. By progress report 2 we will have layout simulation results to confirm this.

As stated earlier an important goal for us was to be able to directly chain multiple INTRANEX chips together. Our current design achieves this and an example chain showing 3 INTRANEXs chained together is shown below. Note that the pin layout in this diagram matches that of the actual layout we plan on implementing.

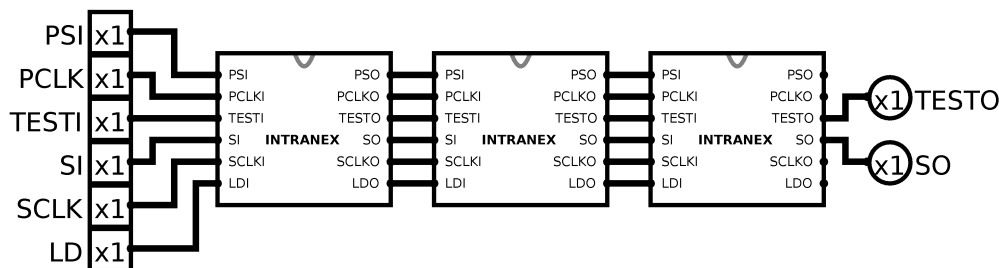


Figure 1.6: 3 INTRANEX Chain

1.4 Block Diagrams

1.4.1 Top Level

A top level block diagram for a 3-bit INTRANEX is shown below. The top module is the PIN and the bottom module is the parallel load shift register. Test mode logic has been excluded to more clearly illustrate the core functionality.

 


Figure 1.7: Top Level Block Diagram (3-Bit Configuration)

1.4.2 Top Level With Test Mode

The same top level diagram is shown with the addition of the test mode logic. The test mode logic simply consists of 3 2:1 multiplexers that redirect the output of the shift register to the input of the PIN and the output of the PIN to what is normally the output of the shift register. In other words, it wires in the PIN between the shifter and the shifters normal output pins.

 


Figure 1.8: Top Level Block Diagram Showing Test Mode Logic (3-Bit Configuration)

1.4.3 Top Level Bit Sliced

The diagram below shows a bit sliced version of the top level diagram shown in Figure 1.7. We can see how each slice is directly connected together with zero interfacing logic as well as the long row-to-row connections as discussed earlier.

 


Figure 1.9: Top Level Bit Sliced Block Diagram (3-Bit Configuration)

1.4.4 Parallel Load Shift Register

Bit-slicing Scheme

Looking at just the shift register we can see that it is a parallel load parallel output shifter that is easily extendable by simply tacking on additional slices.

 


Figure 1.10: Parallel Load Bit-Sliced Shifter Register (3-Bit Configuration)

Bit-Slice

Looking at the internals of a single shift slice we can see that is is just a 2:1 multiplexer and a D Flip Flop. The multiplexer determines if the slice should load either the value from the previous slice (SI) or the parallel input (Z). When LDI is 0 it uses the value of the previous slice and when it is a 1 it uses the parallel load value.

 


Figure 1.11: Parallel Load Shifter Register Bit-Slice

1.4.5 Programmable Interconnect Network

Bit-slicing Scheme

The diagram below shows just the PIN in bit-slice form. One of the design decisions made while determining the slice interconnects was to also pass the PCLK from slice to slice. The alternative was to simply connect each slice's PCLKI to the main PCLKI pin at a higher level. We wanted to avoid as much manual layout as possible so it determined to be easier and cleaner to route the clock in such a way that it would be automatically connected when we layout the slice array.

 


Figure 1.12: Bit-Sliced Programmable Interconnect Network (3-Bit Configuration)

Bit-Slice

The PIN bit-slices, one of which is shown below, is what drive the whole functionality of our chip. WI is the input values bit for the current column. If that bit is set and this slice is configured as 'connected' we want to output a logic high on the Z bus simultaneously. We cannot, however, just simply AND these two values together and attach it to the bus as this would allow for multiple slices to drive or sink the bus. To avoid this we use an OR gate to determine if the slice behind us is outputting a 1. If so we just pass it along. If we want to output a 1 it is also no problem as the OR will accommodate us as well.

 


Figure 1.13: Programmable Interconnect Network Bit-Slice

1.5 VHDL Models

1.5.1 Top Level

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity top is
5      generic(
6          n : integer := 3
7      );
8      port(
9          psi : in  std_logic;
10         pso : out std_logic;
11         pclk : in  std_logic;
12         si : in  std_logic;
13         so : out std_logic;
14         sclk : in  std_logic;
15         ld : in  std_logic;
16         test : in  std_logic;
17     );
18 end top;
19
20 architecture rtl of top is
21
22     -- output of pin
23     signal z : std_logic_vector((n-1) downto 0) := (others => '0');
24     -- parallel output of shifter
25     signal w : std_logic_vector((n-1) downto 0) := (others => '0');
26
27     signal pin_clk : std_logic;
28     signal pin_psi : std_logic;
29     signal pin_pso : std_logic;
30     signal shift_out : std_logic;
31
32 begin
33
34     -- test mode mux connects shifter and pin together
35     test_mux_1 : entity work.mux2x1 port map(pclk, sclk, test, pin_clk);
36     test_mux_2 : entity work.mux2x1 port map(psi, shift_out, test, pin_psi);
37     test_mux_3 : entity work.mux2x1 port map(shift_out, pin_pso, test, so);
38
39     pin : entity work.pin
40     generic map(
41         n => n
42     )
43     port map(
44         clk => pin_clk,
45         psi => pin_psi,
46         pso => pin_pso,
47         z => z,
48         w => w
49     );
50
51     pso <= pin_pso;
52
53     shifter : entity work.shift
54     generic map(
55         n => n
56     )
57     port map(
58         clk => sclk,
59         si => si,
60         so => shift_out,
61         ld => ld,
62         z => z,
63         w => w
64     );
65
66 end rtl;

```

Listing 1.1: Top Level VHDL Module

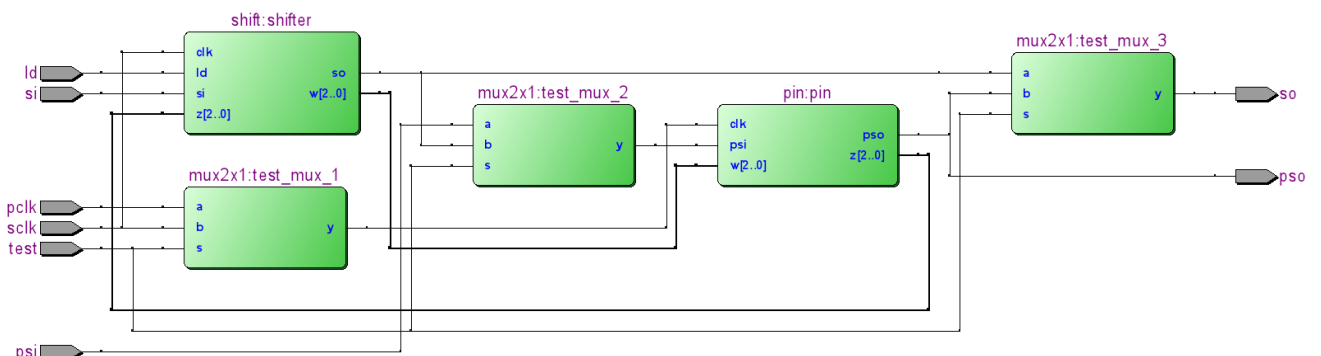


Figure 1.14: Top Level Generated RTL Diagram

1.5.2 PIN

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity pin is
5      generic(
6          n : integer := 3
7      );
8      port(
9          clk : in  std_logic;
10         psi : in  std_logic;
11         pso : out std_logic;
12         z   : out std_logic_vector((n-1) downto 0);
13         w   : in  std_logic_vector((n-1) downto 0)
14     );
15 end pin;
16
17 architecture rtl of pin is
18
19     component pin_slice is
20         port(
21             zi : in  std_logic;
22             qi : in  std_logic;
23             wi : in  std_logic;
24             ci : in  std_logic;
25             zo : out std_logic;
26             qo : out std_logic;
27             wo : out std_logic;
28             co : out std_logic
29         );
30     end component;
31
32     -- carry.array(row, col)
33     type carry_array is array (0 to n, 0 to n) of std_logic;
34     signal zc : carry_array;
35     signal cc : carry_array;
36     signal wc : carry_array;
37     signal qc : carry_array;
38
39     begin
40
41         -- setup first and last inputs for each row
42         z_connect : for i in 0 to n-1 generate
43             zc(i, 0) <= '0';
44             z(i) <= zc(i, n);
45         end generate;
46
47         -- setup first inputs for each column
48         w_connect : for i in 0 to n-1 generate
49             wc(0, i) <= w(i);
50         end generate;
51
52         -- setup row transfer
53         -- (last output of row to first input of next row)
54         r_connect : for i in 0 to n-2 generate
55             qc(i, 0) <= qc(i+1, n);
56             cc(i, 0) <= cc(i+1, n);
57         end generate;
58
59         -- connect external inputs
60         qc(n-1, 0) <= psi;
61         cc(n-1, 0) <= clk;
62         pso <= qc(0, n);
63
64         -- generate the grid of slices
65         pin_z_gen : for zz in 0 to n-1 generate
66             pin_w_gen : for ww in 0 to n-1 generate
67                 pin_i : pin_slice port map(
68                     zi => zc(zz, ww),
69                     qi => qc(zz, ww),
70                     wi => wc(zz, ww),
71                     ci => cc(zz, ww),
72                     zo => zc(zz, ww+1),
73                     qo => qc(zz, ww+1),
74                     wo => wc(zz+1, ww),
75                     co => cc(zz, ww+1)
76                 );
77             end generate;
78         end generate;
79
80     end rtl;

```

Listing 1.2: PIN VHDL Module

 


Figure 1.15: Pin Generated RTL Diagram

1.5.3 PIN Slice

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity pin_slice is
5      port(
6          zi : in std_logic;
7          qi : in std_logic;
8          wi : in std_logic;
9          ci : in std_logic;
10         zo : out std_logic;
11         qo : out std_logic;
12         wo : out std_logic;
13         co : out std_logic;
14     );
15 end pin_slice;
16
17 architecture rtl of pin_slice is
18
19     signal g1_o : std_logic := '0';
20     signal g2_o : std_logic := '0';
21
22 begin
23
24     g1 : entity work.dffposx1 port map(ci, qi, g1_o);
25     g2 : entity work.aoi21x1 port map(wi, g1_o, zi, g2_o);
26     g3 : entity work.invx1 port map(g2_o, zo);
27
28     -- pass through
29     co <= ci;
30     wo <= wi;
31     qo <= g1_o;
32
33 end rtl;

```

Listing 1.3: PIN Slice VHDL Module

 


Figure 1.16: Pin Slice Generated RTL Diagram

1.5.4 Shifter

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity shift is
5     generic(
6         n : integer := 3
7     );
8     port(
9         clk : in  std_logic;
10        ld  : in  std_logic;
11        si  : in  std_logic;
12        so  : out std_logic;
13        z   : in  std_logic_vector((n-1) downto 0);
14        w   : out std_logic_vector((n-1) downto 0)
15    );
16 end shift;
17
18 architecture rtl of shift is
19
20     component shift_slice
21     port(
22         clki : in  std_logic;
23         clko : out std_logic;
24         ldi  : in  std_logic;
25         ldo  : out std_logic;
26         si   : in  std_logic;
27         so   : out std_logic;
28         z    : in  std_logic
29     );
30 end component;
31
32 -- vector to hold values between slices
33 signal c_so : std_logic_vector(n downto 0) := (others => '0');
34 signal c_clk : std_logic_vector(n downto 0) := (others => '0');
35 signal c_ld : std_logic_vector(n downto 0) := (others => '0');
36
37 begin
38
39     -- input of slice 0 comes from module input
40     c_so(0) <= si;
41     c_ld(0) <= ld;
42     c_clk(0) <= clk;
43
44     -- final shift output comes from output of last slice
45     so <= c_so(n);
46
47     -- generate N slices
48     shift_gen : for i in 0 to n-1 generate
49         shift_i : shift_slice port map(
50             clki => c_clk(i),
51             clko => c_clk(i+1),
52             ldi  => c_ld(i),
53             ldo  => c_ld(i+1),
54             si   => c_so(i),
55             so   => c_so(i+1),
56             z    => z(i)
57         );
58     end generate;
59
60     -- connect the output of each slice to parallel output vector
61     connect : for i in 0 to n-1 generate
62         w(i) <= c_so(i+1);
63     end generate;
64
65 end rtl;

```

Listing 1.4: Parallel Load Shifter VHDL Module

 


Figure 1.17: Shifter Generated RTL Diagram

1.5.5 Shifter Slice

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity shift_slice is
5      port(
6          clki : in  std_logic;
7          clko : out std_logic;
8          ldi  : in  std_logic;
9          ldo  : out std_logic;
10         si   : in  std_logic;
11         so   : out std_logic;
12         z    : in  std_logic
13     );
14 end shift_slice;
15
16 architecture rtl of shift_slice is
17     signal g1_o : std_logic := '0';
18
19 begin
20
21     g1 : entity work.mux2x1 port map(si, z, ldi, g1_o);
22     g2 : entity work.dffposx1 port map(clki, g1_o, so);
23
24     -- pass through
25     clko <= clki;
26     ldo <= ldi;
27
28 end rtl;

```

Listing 1.5: Parallel Load Shifter Slice VHDL Module

 


Figure 1.18: Shifter Slice Generated RTL Diagram

1.5.6 Gates

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity aoi21x1 is
5      generic(delay : time := 0 ps);
6      port(
7          a : in std_logic;
8          b : in std_logic;
9          c : in std_logic;
10         y : out std_logic
11     );
12 end aoi21x1;
13
14 architecture rtl of aoi21x1 is begin
15     process(a, b, c) begin
16         y <= not ((a and b) or c) after delay;
17     end process;
18 end rtl;

```

Listing 1.6: AOI21X1 VHDL Module

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity dffposx1 is
5      generic(delay : time := 0 ps);
6      port(
7          c : in std_logic;
8          d : in std_logic;
9          q : out std_logic := '0'
10     );
11 end dffposx1;
12
13 architecture rtl of dffposx1 is begin
14     process(c) begin
15         if rising_edge(c) then
16             q <= d after delay;
17         end if;
18     end process;
19 end rtl;

```

Listing 1.7: DFFPOSX1 VHDL Module

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity invx1 is
5      generic(delay : time := 0 ps);
6      port(
7          a : in std_logic;
8          y : out std_logic
9     );
10 end invx1;
11
12 architecture rtl of invx1 is begin
13     y <= not a after delay;
14 end rtl;

```

Listing 1.8: IN VX1 VHDL Module

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity mux2x1 is
5      generic(delay : time := 0 ps);
6      port(
7          a : in std_logic;
8          b : in std_logic;
9          s : in std_logic;
10         y : out std_logic
11     );
12 end mux2x1;
13
14 architecture rtl of mux2x1 is begin
15     process(a, b, s) begin
16         if (s = '1') then
17             y <= b after delay;
18         else
19             y <= a after delay;
20         end if;
21     end process;
22 end rtl;

```

Listing 1.9: MUX2X1 VHDL Module

1.6 VHDL Test Benches

1.6.1 Top Level Functional

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use std.textio.all;
4  use work.txt_util.all;
5
6  entity top_tb is
7      generic(
8          stim_file : string := "vectors.3.bit.sim"
9      );
10 end top_tb;
11
12 architecture tb_rtl of top_tb is
13
14     constant n : integer := 3;
15
16     signal psi : std_logic := '0';
17     signal pso : std_logic;
18     signal pclk : std_logic := '0';
19     signal si : std_logic := '0';
20     signal so : std_logic;
21     signal sclk : std_logic := '0';
22     signal ld : std_logic := '0';
23     signal test : std_logic := '0';
24
25     component top
26     generic(
27         n : integer := 3
28     );
29     port(
30         psi : in std_logic;
31         pso : out std_logic;
32         pclk : in std_logic;
33         si : in std_logic;
34         so : out std_logic;
35         sclk : in std_logic;
36         ld : in std_logic;
37         test : in std_logic
38     );
39 end component;
40
41 signal pin_vector : std_logic_vector((n*n)-1 downto 0);
42 signal shift_vector : std_logic_vector(n-1 downto 0);
43 signal result_vector : std_logic_vector(n-1 downto 0);
44
45 file stimulus : TEXT open read_mode is stim_file;
46
47 begin
48
49     uut : top
50     generic map(
51         n => n
52     )
53     port map(
54         psi => psi,
55         pso => pso,
56         pclk => pclk,
57         si => si,
58         so => so,
59         sclk => sclk,
60         ld => ld,
61         test => test
62     );
63
64     process
65
66         procedure clock_shifter is begin
67             sclk <= '1';
68             wait for 20 ns;
69             sclk <= '0';
70             wait for 20 ns;
71         end procedure clock_shifter;
72
73         procedure clock_pin is begin
74             pclk <= '1';
75             wait for 20 ns;
76             pclk <= '0';
77             wait for 20 ns;
78         end procedure clock_pin;
79
80         variable l : line;
81         variable pin_str : string(1 to n*n);
82         variable shf_str : string(1 to n);
83
84     begin
85
86         while not endfile(stimulus) loop
87
88             -- load stimulus for this test
89             readline(stimulus, l); read(l, pin_str);
90             pin_vector <= to_std_logic_vector(pin_str);
91
92             readline(stimulus, l); read(l, shf_str);
93             shift_vector <= to_std_logic_vector(shf_str);
94
95             readline(stimulus, l); read(l, shf_str);
96             result_vector <= to_std_logic_vector(shf_str);
97
98             wait for 100 ns;
99

```

```

100      -- clock in the pin
101      for i in 0 to (n*n)-1 loop
102          psi <= pin_vector(i);
103          wait for 20 ns;
104          clock_pin;
105      end loop;
106
107      -- clock in the value
108      for i in 0 to n-1 loop
109          si <= shift_vector(i);
110          wait for 20 ns;
111          clock_shifter;
112      end loop;
113
114      -- pull latch high so the first result
115      -- loop will trigger the latch
116      ld <= '1';
117      wait for 20 ns;
118
119      -- clock out result and check it
120      for i in 0 to n-1 loop
121          clock_shifter;
122          assert so = result_vector(i) report "Test Failed!";
123          ld <= '0';
124          wait for 20 ns;
125      end loop;
126
127      end loop;
128
129      report "Test Complete" severity note;
130      wait;
131
132      end process;
133
134      end tb_rtl;

```

Listing 1.10: Top Level VHDL Test Bench

We decided to write a small Python script to generate the expected output vector for all possible PIN configurations and input values. Our test bench then runs through all of these vectors and checks if the output vector from our VHDL design matches the known output.

```

1  N = 3
2
3  out = open("vectors.%d.bit.sim"%N, "w")
4
5  # loop through all possible pins and shift values
6  for pin in range(2*(N*N)):
7      for shift in range(2*N):
8
9          # get bit strings
10         pin_bits = bin(pin).replace("0b", "").zfill(N*N)
11         shift_bits = bin(shift).replace("0b", "").zfill(N)
12         result_bits = ["0"]*N
13
14         # calculate the expected result
15         for z in range(N):
16             for w in range(N):
17                 if pin_bits[(N-1-z)*N+w] == "1" and shift_bits[w] == "1":
18                     result_bits[z] = "1"
19
20         # writeout results
21         out.write("%s\n" % pin_bits)
22         out.write("%s\n" % shift_bits)
23         out.write("%s\n" % "".join(result_bits))
24
25  out.close()

```

Listing 1.11: Python Vector Generator

1.6.2 Top Level Test Mode

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity top_test_tb is
5  end top_test_tb;
6
7  architecture tb_rtl of top_test_tb is
8
9      constant n : integer := 3;
10
11     signal psi : std_logic := '0';
12     signal pso : std_logic;
13     signal pclk : std_logic := '0';
14     signal si : std_logic := '0';
15     signal so : std_logic;
16     signal sclk : std_logic := '0';
17     signal ld : std_logic := '0';
18     signal test : std_logic := '0';
19
20     component top
21     generic(
22         n : integer := n
23     );
24     port(
25         psi : in std_logic;
26         pso : out std_logic;
27         pclk : in std_logic;
28         si : in std_logic;
29         so : out std_logic;
30         sclk : in std_logic;
31         ld : in std_logic;
32         test : in std_logic
33     );
34     end component;
35
36 begin
37
38     uut : top
39     generic map(
40         n => n
41     )
42     port map(
43         psi => psi,
44         pso => pso,
45         pclk => pclk,
46         si => si,
47         so => so,
48         sclk => sclk,
49         ld => ld,
50         test => test
51     );
52
53     process
54     procedure clock is begin
55         sclk <= '1';
56         wait for 20 ns;
57         sclk <= '0';
58         wait for 20 ns;
59     end procedure clock;
60     begin
61
62         wait for 20 ns;
63
64         -- pull test line high to enable test mode
65         test <= '1';
66
67         -- clock in a '1'
68         si <= '1';
69         wait for 20 ns;
70         clock;
71
72         -- clock in a '0'
73         si <= '0';
74         wait for 20 ns;
75         clock;
76
77         -- push the pulse through till just before the last FF
78         -- (n*n)+n == number of flip flops
79         -- 2 == we already did two clocks
80         -- 1 == we want to stop before before final output
81         for i in 1 to (n*n)+n-2-1 loop
82             clock;
83         end loop;
84
85         -- check to make sure the bit in front of the pulse is 0
86         assert so = '0' report "Bit leading pulse not 0";
87         clock;
88         -- check to make sure the pulse is 1
89         assert so = '1' report "Pulse is not 1";
90         clock;
91         -- check to make sure the bit behind pulse is 0
92         assert so = '0' report "Bit trailing pulse not 0";
93         clock;
94
95         report "Test Complete" severity note;
96         wait;
97     end process;
98
99 end tb_rtl;

```

Listing 1.12: Top Level Test Mode VHDL Test Bench

1.6.3 PIN Slice

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity pin_slice_tb is
5  end pin_slice_tb;
6
7  architecture tb_rtl of pin_slice_tb is
8
9      signal zi : std_logic := '0';
10     signal qi : std_logic := '0';
11     signal wi : std_logic := '0';
12     signal ci : std_logic := '0';
13     signal zo : std_logic;
14     signal qo : std_logic;
15     signal wo : std_logic;
16     signal co : std_logic;
17
18     component pin_slice
19     port(
20         zi : in std_logic;
21         qi : in std_logic;
22         wi : in std_logic;
23         ci : in std_logic;
24         zo : out std_logic;
25         qo : out std_logic;
26         wo : out std_logic;
27         co : out std_logic
28     );
29     end component;
30
31 begin
32
33     uut : pin_slice
34     port map(
35         zi => zi,
36         qi => qi,
37         wi => wi,
38         ci => ci,
39         zo => zo,
40         qo => qo,
41         wo => wo,
42         co => co
43     );
44
45     process
46         type pattern_type is record
47             -- inputs
48             zi, qi, wi : std_logic;
49             -- output
50             zo : std_logic;
51         end record;
52
53         type pattern_array is array (natural range <>) of pattern_type;
54         constant patterns : pattern_array :=
55             -- zi  qi  wi  zo
56             (( '0', '0', '0', '0'),
57              ('0', '0', '1', '0'),
58              ('0', '1', '0', '0'),
59              ('0', '1', '1', '1'),
60              ('1', '0', '0', '1'),
61              ('1', '0', '1', '1'),
62              ('1', '1', '0', '1'),
63              ('1', '1', '1', '1'));
64
65     begin
66         -- check each pattern
67         for i in patterns'range loop
68
69             -- set the inputs
70             zi <= patterns(i).zi;
71             qi <= patterns(i).qi;
72             wi <= patterns(i).wi;
73             wait for 10 ns;
74
75             -- pulse the clock and check clock passthrough
76             ci <= '1';
77             wait for 10 ns;
78             assert co = '1' report "CO does not equal 1" severity error;
79             ci <= '0';
80             wait for 10 ns;
81             assert co = '0' report "CO does not equal 0" severity error;
82
83             -- check the outputs
84             assert qo = patterns(i).qi report "QI not equal QO" severity error;
85             assert zo = patterns(i).zo report "ZO does not match pattern" severity error;
86
87         end loop;
88
89         report "Test Complete" severity note;
90         wait;
91
92     end process;
93
94 end tb_rtl;

```

Listing 1.13: PIN Slice VHDL Test Bench

1.6.4 Shifter Slice

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity shift_slice_tb is
5  end shift_slice_tb;
6
7  architecture tb_rtl of shift_slice_tb is
8
9      signal clki    : std_logic := '0';
10     signal clko    : std_logic;
11     signal ldi     : std_logic := '0';
12     signal ldo     : std_logic;
13     signal si      : std_logic := '0';
14     signal so      : std_logic;
15     signal z       : std_logic := '0';
16
17     component shift_slice is
18     port(
19         clki : in  std_logic;
20         clko : out std_logic;
21         ldi  : in  std_logic;
22         ldo  : out std_logic;
23         si   : in  std_logic;
24         so   : out std_logic;
25         z    : in  std_logic
26     );
27 end component;
28
29 begin
30
31     uut : shift_slice
32     port map(
33         clki => clki,
34         clko => clko,
35         ldi  => ldi,
36         ldo  => ldo,
37         si   => si,
38         so   => so,
39         z    => z
40     );
41
42     process
43         type pattern_type is record
44             -- inputs
45             ldi, z, si : std_logic;
46             -- output
47             so : std_logic;
48         end record;
49
50         type pattern_array is array (natural range <>) of pattern_type;
51         constant patterns : pattern_array :=
52             -- ldi, z, si, so
53             ((('0','0','0','0'),
54              ('0','0','1','1'),
55              ('0','1','0','0'),
56              ('0','1','1','1'),
57              ('1','0','0','0'),
58              ('1','0','1','0'),
59              ('1','1','0','1'),
60              ('1','1','1','1')));
61
62     begin
63         -- check each pattern
64         for i in patterns'range loop
65
66             -- set the inputs
67             ldi <= patterns(i).ldi;
68             z  <= patterns(i).z;
69             si <= patterns(i).si;
70             wait for 10 ns;
71
72             -- pulse the clock and check clock passthrough
73             clki <= '1';
74             wait for 10 ns;
75             assert clko = '1' report "SCLKO does not equal 1" severity error;
76             assert ldo = patterns(i).ldi report "SCLKO does not equal 1" severity error;
77             clki <= '0';
78             wait for 10 ns;
79             assert clko = '0' report "SCLKO does not equal 0" severity error;
80             assert ldo = patterns(i).ldi report "SCLKO does not equal 1" severity error;
81
82             -- check the output
83             assert so = patterns(i).so report "SO is incorrect" severity error;
84
85         end loop;
86
87         report "Test Complete" severity note;
88         wait;
89
90     end process;
91
92 end tb_rtl;

```

Listing 1.14: Parallel Load Shifter Slice VHDL Test Bench

1.7 VHDL Test Bench Results

1.7.1 Top Level Functional

While our top level functional testbench is completely automated and does an exhaustive test on all possible inputs an example waveform is shown below. We can first see that we clock in a PIN configuration vector of 000001000 which enables slice Z1W2. We then shift in a value of 001. Given these input vectors we expect the output vector to be 010. We can see from the waveform below that we achieve the expected result.

 


Figure 1.19: Top Level Functional Test Bench Waveform

1.7.2 Top Level Test Mode

Our top level test mode testbench is also completely automated. For this test we simply send a pulse through all the flip flops and count the number of clock cycles it takes for the pulse to come out the other end. For a 3-Bit configuration there are $3 \times 3 + 3$ flip flops so we expect the pulse to appear at the output after 12 clock pulses. We can see from the waveform below that we achieve the expected output.

 


Figure 1.20: Top Level Test Mode Test Bench Waveform

1.8 Work Division

Task	Person
Pinout Diagram	Both
Explanation of Functionality	Both
Design Decisions	Both
Top Level Block Diagrams	Both
Shifter Block Diagrams	Qi
PIN Block Diagrams	Thrun
VHDL Shifter+TB	Qi
VHDL PIN+TB	Qi
VHDL Top+TB	Thrun
VHDL Top Test Mode TB	Thrun

Table 1.2: Task Assignment

Chapter 2

Progress Report 2

2.1 Slice Layouts

2.1.1 PIN Slice Layout

The PIN slice layout consists of 3 cells from the provided library. They were arranged as to provided maximum material density and uniformity among the power rails. The connections in and out of the slice are arranged such that slices can be directly patterned together with little to no additional connections at a higher level.

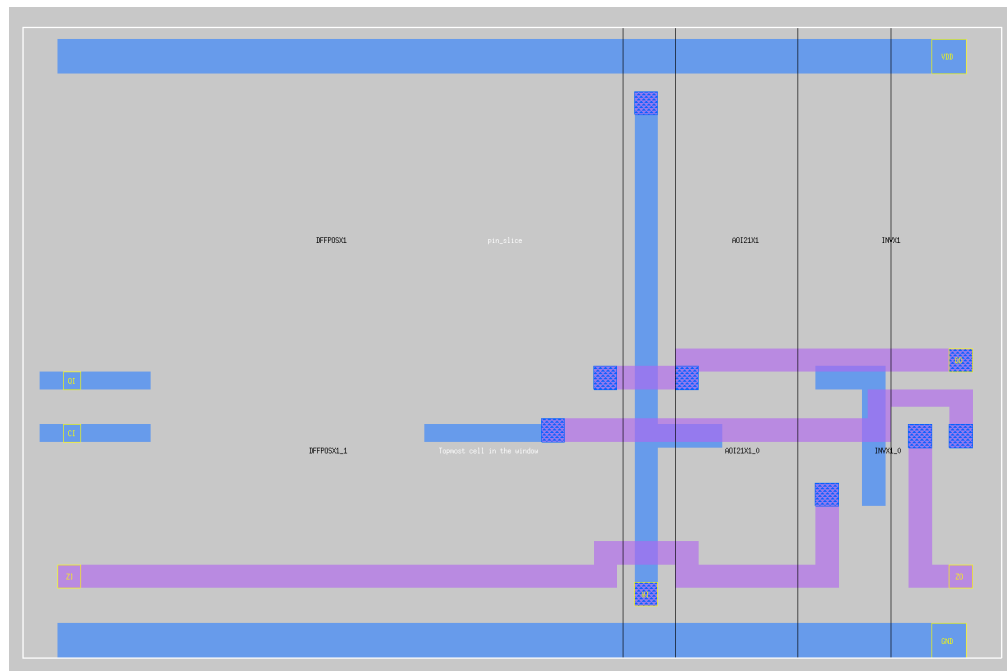


Figure 2.1: PIN Slice Layout

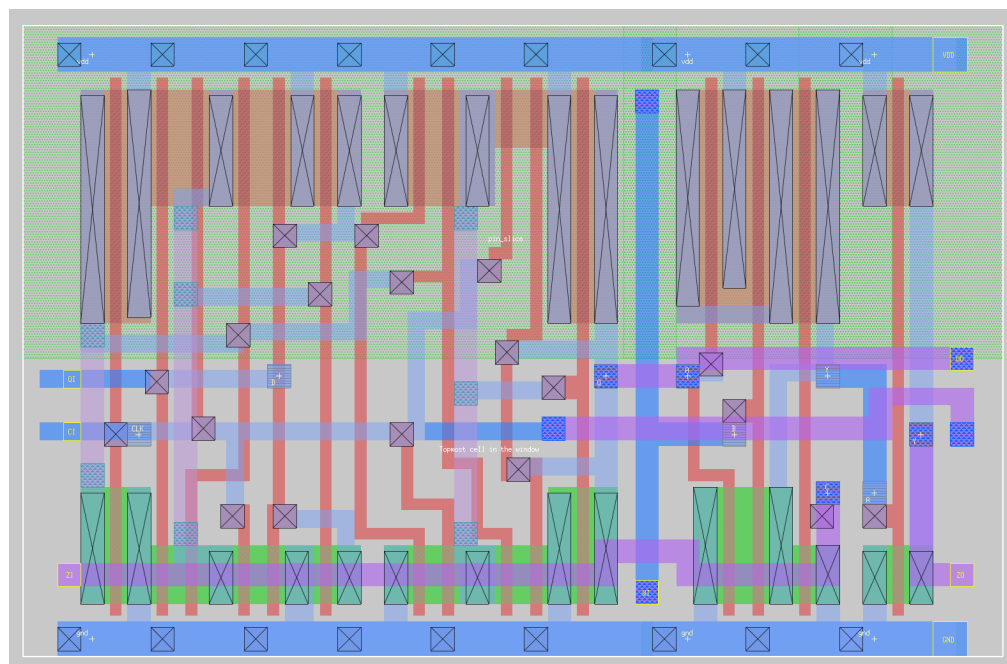


Figure 2.2: PIN Slice Layout Internal

2.1.2 Shift Slice Layout

Like the PIN slice, the Shift slice layout consists of 3 cells from the provided library. Again, we chose to keep a linear layout to maintain a uniform power rail between slices. Also, like the PIN slice, the connections in and out of this slice are laid out in such a manner that allows for direct patterning of slices with no additional work required.

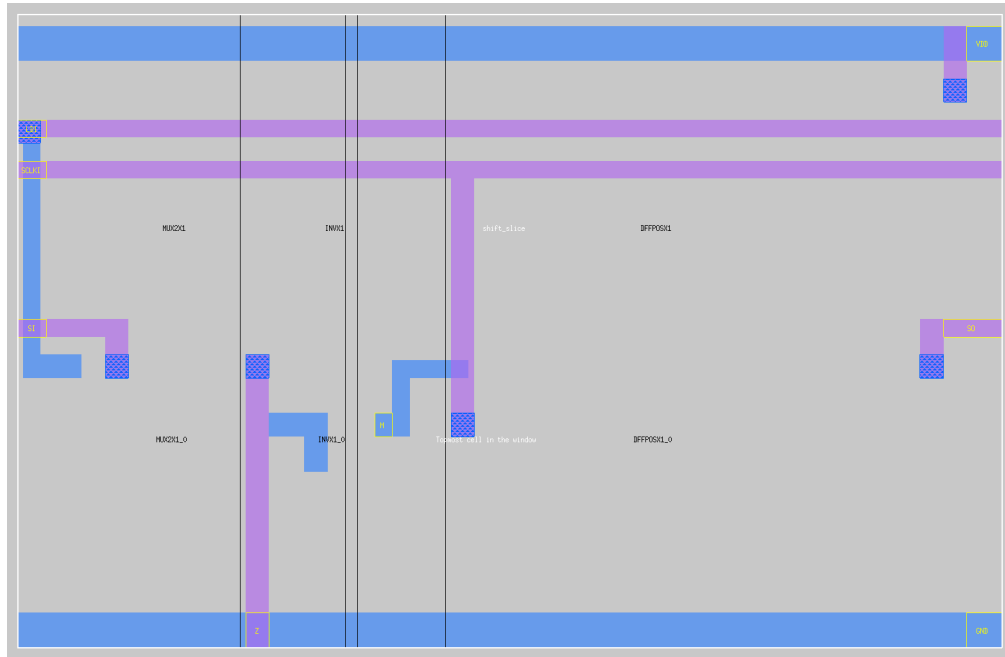


Figure 2.3: PIN Slice Layout

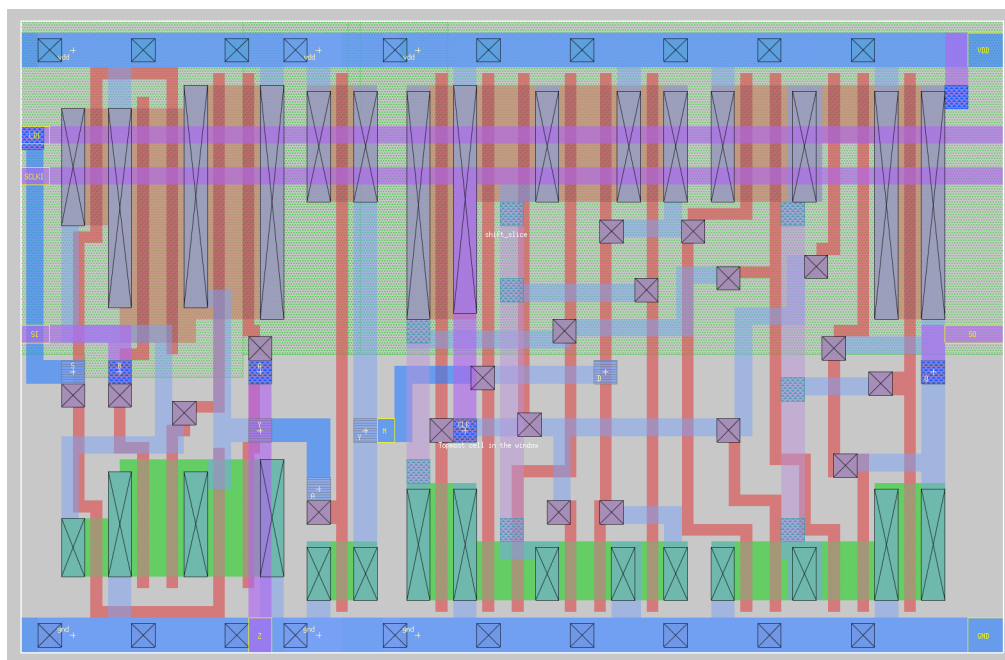


Figure 2.4: PIN Slice Layout Internal

2.2 Slice IRSIM Results

2.2.1 PIN Slice IRSIM Results

In order to test the PIN slice functionally a Python script was developed that translates our VHDL testbench patterns into a IRSIM command file. The output CMD file is not included here because of its length and the fact that it can be inferred from the Python script shown below.

```

1  with open("pin_slice.cmd", "w") as f:
2
3      f.write("stepsize 10\n")
4      f.write("logfile pin_slice.log\n")
5      f.write("h VDD\n")
6      f.write("l GND\n")
7      f.write("vector CLK Cl\n")
8      f.write("clock CLK 0 1\n")
9      f.write("ana Cl Zi Qi Wi Zo Qo\n")
10     f.write("w  Cl Zi Qi Wi Zo Qo\n")
11
12     # zi qi wi zo
13     patterns = (
14         ('l','l','l','l'),
15         ('l','l','h','l'),
16         ('l','h','l','l'),
17         ('l','h','h','h'),
18         ('h','l','l','h'),
19         ('h','l','h','h'),
20         ('h','h','l','h'),
21         ('h','h','h','h')
22     )
23
24     for zi, qi, wi, zo in patterns:
25         f.write("%s Zi\n" % zi)
26         f.write("%s Qi\n" % qi)
27         f.write("%s Wi\n" % wi)
28         f.write("c CLK\n")

```

Listing 2.1: Python PIN Slice IRSIM CMD File Generator

The resulting IRSIM waveform, shown below, illustrates that we achieve correct functional behavior for our slice layout.

 


Figure 2.5: PIN Slice IRSIM Functional Results

The critical path through the PIN slice is highlighted in red in the diagram below. Knowing this path we constructed a simple CMD file to toggle the `qi` pin high and low on two consecutive clock cycles. This gives us a rising and falling edge through the critical path that we were able to measure using the `PATH` command in IRSIM.

 


Figure 2.6: PIN Slice Critical Path

The textual output from IRSIM is shown below:

```

Q0=0 WI=1 QI=0 ZI=0 Z0=0 CI=1
time = 20.000ns
Q0=1 WI=1 QI=1 ZI=0 Z0=1 CI=1
time = 40.000ns
critical path for last transition of Z0:
  CI -> 1 @ 30.000ns , node was an input
  DFFPOSX1_1/a_66_6# -> 0 @ 30.141ns (0.141ns)
  Q0 -> 1 @ 30.230ns (0.089ns)
  INVX1_0/A -> 0 @ 30.285ns (0.055ns)
  Z0 -> 1 @ 30.286ns (0.001ns)
Q0=0 WI=1 QI=0 ZI=0 Z0=0 CI=1
time = 60.000ns
critical path for last transition of Z0:
  CI -> 1 @ 50.000ns , node was an input
  DFFPOSX1_1/a_2_6# -> 0 @ 50.039ns (0.039ns)
  DFFPOSX1_1/a_66_6# -> 1 @ 50.198ns (0.159ns)
  Q0 -> 0 @ 50.290ns (0.092ns)
  INVX1_0/A -> 1 @ 50.347ns (0.057ns)
  Z0 -> 0 @ 50.348ns (0.001ns)

```

Figure 2.7: PIN Slice IRSIM Critical Path Delay

Looking at the output we can see the two delays of the critical path. The first of the two delays is the output value going from a 0 to a 1 and the second is the output going from a 1 to a 0. The table below tabulates the two delays and indicates that the falling edge delay was the worse of the two.

State Change	Delay	
0	0.286n	
1	0.348n	WORST

Table 2.1: PIN Slice IRSIM Critical Path Delays

2.2.2 Shift Slice IRSIM Results

Similarly to the PIN slice, for the Shift Slice we used the same Python script to generate a CMD file that matched our VHDL testbench patterns. The script is shown below:

```

1  with open("shift_slice.cmd", "w") as f:
2
3      f.write("stepsize 10\n")
4      f.write("logfile shift_slice.log\n")
5      f.write("h VDD\n")
6      f.write("l GND\n")
7      f.write("vector CLK SCLKI\n")
8      f.write("clock CLK 0 1\n")
9      f.write("ana SCLKI LDI SI Z SO\n")
10     f.write("w SCLKI LDI SI Z SO\n")
11
12     # ldi z si so
13     patterns = (
14         ('l', 'l', 'l', 'l'),
15         ('l', 'l', 'h', 'h'),
16         ('l', 'h', 'l', 'l'),
17         ('l', 'h', 'h', 'h'),
18         ('h', 'l', 'l', 'l'),
19         ('h', 'l', 'h', 'l'),
20         ('h', 'h', 'l', 'h'),
21         ('h', 'h', 'h', 'h')
22     )
23
24     for ldi, z, si, so in patterns:
25         f.write("%s LDI\n" % ldi)
26         f.write("%s Z\n" % z)
27         f.write("%s SI\n" % si)
28         f.write("c CLK\n")

```

Listing 2.2: Python Shift Slice IRSIM CMD File Generator

Looking at the results we can see that our Shift Slice performs as expected and matches our VHDL simulations.

 


Figure 2.8: Shift Slice IRSIM Functional Results

The critical path through the shift slice is highlighted in red in the diagram below. Again, knowing this path we constructed a simple CMD file to drive a pulse through the path.

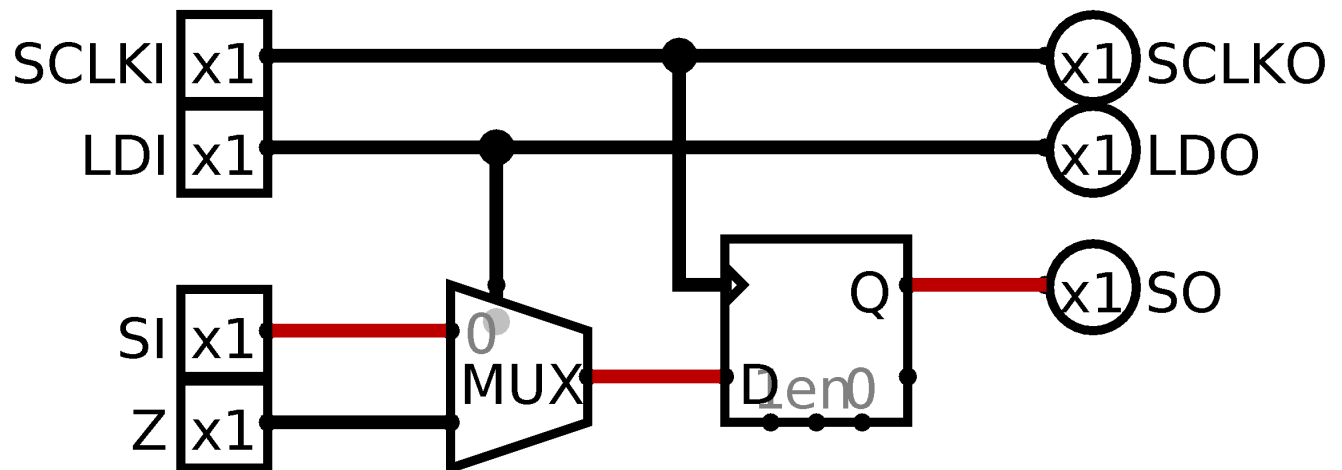


Figure 2.9: Shift Slice Critical Path

The textual output from IRSIM, shown below, provides us with two critical path delays one for the rising edge of the output and one for the falling edge.

```

S0=0 Z=0 SI=0 LDI=0 SCLKI=1
time = 20.000ns
S0=1 Z=0 SI=1 LDI=0 SCLKI=1
time = 40.000ns
critical path for last transition of S0:
  SCLKI -> 1 @ 30.000ns , node was an input
  DFFPOSX1_0/a_66_6# -> 0 @ 30.141ns (0.141ns)
  S0 -> 1 @ 30.181ns (0.040ns)
S0=0 Z=0 SI=0 LDI=0 SCLKI=1
time = 60.000ns
critical path for last transition of S0:
  SCLKI -> 1 @ 50.000ns , node was an input
  DFFPOSX1_0/a_2_6# -> 0 @ 50.040ns (0.040ns)
  DFFPOSX1_0/a_66_6# -> 1 @ 50.200ns (0.160ns)
  S0 -> 0 @ 50.242ns (0.042ns)

```

Figure 2.10: Shift Slice IRSIM Critical Path Delay

Looking at the output we can see that again the falling edge has a greater propagation delay through the path. The table below summarizes the results for this slice.

State Change	Delay
0	0.181n
1	0.242n WORST

Table 2.2: Shift Slice IRSIM Critical Path Delays

2.3 Slice Spice Results

2.3.1 PIN Slice Spice Results

We wanted to be able to functionally test our slices in HSpice in addition to analyzing the propagation delay. To do this another Python script was written that took our test patterns and wrote out the required Piecewise Linear (PWL) statements to generate them.

```

1  # zi qi wi zo
2  patterns = (
3      ('0', '0', '0', '0'),
4      ('0', '0', '5', '0'),
5      ('0', '5', '0', '0'),
6      ('0', '5', '5', '5'),
7      ('5', '0', '0', '5'),
8      ('5', '0', '5', '5'),
9      ('5', '5', '0', '5'),
10     ('5', '5', '5', '5')
11 )
12
13 with open("pin_slice_all.sp", "w") as f:
14
15     f.write("* Pin Slice Test All\n")
16
17     f.write(".include ../../models/model.t36s.sp\n")
18     f.write(".include ../magic/pin_slice.spice\n")
19
20     for n in ("zi", "ci", "qi", "wi", "zo", "qo"):
21         f.write(".ic v(%s) = 0\n" % n)
22
23     f.write("VDD vdd gnd 5V\n")
24
25     f.write("Vsciki ci gnd PULSE(0V 5V 10n 0 0 10n 20n)\n")
26
27     o_zi = ""
28     o_qi = ""
29     o_wi = ""
30
31     for i, (zi, qi, wi, zo) in enumerate(patterns):
32         o_zi += "%dn %sV %fn %sV " % (i*20, zi, (i+1)*20-0.001, zi)
33         o_qi += "%dn %sV %fn %sV " % (i*20, qi, (i+1)*20-0.001, qi)
34         o_wi += "%dn %sV %fn %sV " % (i*20, wi, (i+1)*20-0.001, wi)
35
36     f.write("Vzi zi gnd PWL(%s)\n" % o_zi)
37     f.write("Vqi qi gnd PWL(%s)\n" % o_qi)
38     f.write("Vwi wi gnd PWL(%s)\n" % o_wi)
39
40     f.write(".option post\n")
41     f.write(".tran 0.01n %dn\n" % (len(patterns)*20))
42     f.write(".end\n")

```

Listing 2.3: Python PIN Slice Spice File Generator

In the figure below we can see the result of our functional Spice test. As you can see, it again matches our expected functionality once again proving the slice is operating correctly.

 


Figure 2.11: PIN Slice Spice Functional Results

In order to measure the critical path delay the patterns in the above Python program were modified to simply toggle the input line **QI**. The resulting output was then measured against the input clock **CI** to obtain the delays for both rising and falling edges.

 


Figure 2.12: PIN Slice Spice Critical Path Delay

The delay times for each of these state changes is tabulated below.

State Change	Delay	
0	0.638n	
1	0.792n	WORST

Table 2.3: PIN Slice Spice Critical Path Delays

2.3.2 Shift Slice Spice Results

Similarly to the PIN slice spice tests we again wanted to be able to test the logical functionality of our slice in HSpice. The same Python script was utilized with a few tweaks to the variable names and pattern definitions in order to match this slice.

```

1  # ldi z si so
2  patterns = (
3      ('0', '0', '0', '0'),
4      ('0', '0', '5', '5'),
5      ('0', '5', '0', '0'),
6      ('0', '5', '5', '5'),
7      ('5', '0', '0', '0'),
8      ('5', '0', '5', '0'),
9      ('5', '5', '0', '5'),
10     ('5', '5', '5', '5')
11 )
12
13 with open("shift_slice_all.sp", "w") as f:
14
15     f.write("* Shift Slice Test All\n")
16
17     f.write(".include ../../models/model.t36s.sp\n")
18     f.write(".include ../magic/shift_slice.spice\n")
19
20     for n in ("ldi", "z", "si", "so", "sclki"):
21         f.write(".ic v(%s) = 0\n" % n)
22
23     f.write("VDD vdd gnd 5V\n")
24
25     f.write("Vsciki SCLKI gnd PULSE(0V 5V 10n 0 0 10n 20n)\n")
26
27     o_ldi = ""
28     o_z = ""
29     o_si = ""
30
31     for i, (ldi, z, si, so) in enumerate(patterns):
32         o_ldi += "%dn %sV %fn %sV " % (i*20, ldi, (i+1)*20-0.001, ldi)
33         o_z += "%dn %sV %fn %sV " % (i*20, z, (i+1)*20-0.001, z)
34         o_si += "%dn %sV %fn %sV " % (i*20, si, (i+1)*20-0.001, si)
35
36     f.write("Vldi ldi gnd PWL(%s)\n" % o_ldi)
37     f.write("Vz z gnd PWL(%s)\n" % o_z)
38     f.write("Vsi si gnd PWL(%s)\n" % o_si)
39
40     f.write(".option post\n")
41     f.write(".tran 0.01n %dn\n" % (len(patterns)*20))
42     f.write(".end\n")

```

Listing 2.4: Python Shift Slice Spice File Generator

From the output waveform below we can see that our slice performed as we expected at a logical level.

 


Figure 2.13: Shift Slice Spice Functional Results

To obtain the delays the input pattern was modified to send a single pulse through the critical path. The output was then referenced to the input clock in order to measure the propagation delay of each edge.

 


Figure 2.14: Shift Slice Spice Critical Path Delay

The delays of the rising and falling edges are tabulated below.

State Change	Delay	
0	0.316n	
1	0.455n	WORST

Table 2.4: Shift Slice Spice Critical Path Delays

2.4 Gate Spice Results

In order to figure out the worst case delay of each gate we generate an exhaustive list of input patterns that toggle the gate inputs in every such state that results in the outputs changing. With this we are trying to find the input state change that causes the worst case delay. We then measure each delay using the `.measure` directive and look for worst delay time.

2.4.1 DFFPOSX1 Spice Results

```

1 patterns = ("0", "5", "0")
2
3 with open("dffposx1.test.sp", "w") as f:
4
5     f.write("* DFFPOSX1 Test\n")
6
7     f.write(".include ../../models/model_t36s.sp\n")
8     f.write(".include ../magic/DFFPOSX1.spice\n")
9
10    for n in ("clk", "d", "q"):
11        f.write(".ic v(%s) = 0\n" % n)
12
13    f.write("V1 vdd gnd 5V\n")
14
15    f.write("Vclk clk gnd PULSE(0V 5V 10n 0 0 10n 20n)\n")
16
17    o.d = ""
18
19    for i, d in enumerate(patterns):
20        o.d += "%dn %sV %fn %sV " % (i*20, d, (i+1)*20-0.001, d)
21
22    f.write("Vd d gnd PWL(%s)\n" % o.d)
23
24    f.write(".option post\n")
25    f.write(".tran 0.01n %dn\n" % (len(patterns)*20))
26    f.write(".meas tran delay_0 when v(q)=2.5 td=5n cross=1\n")
27    f.write(".meas tran delay_1 when v(q)=2.5 td=5n cross=2\n")
28    f.write(".end\n")

```

Listing 2.5: Python DFFPOSX1 Spice File Generator

 


Figure 2.15: DFFPOSX1 Spice Results

State Change	Delay	
0	0.3011n	
1	0.4257n	WORST

Table 2.5: DFFPOSX1 Delays

2.4.2 AOI21X1 Spice Results

```

1 import itertools
2
3 # C A B Y
4 patterns = (
5     ('0', '0', '0', '5'),
6     ('0', '0', '5', '5'),
7     ('0', '5', '0', '5'),
8     ('0', '5', '5', '0'),
9     ('5', '0', '0', '0'),
10    ('5', '0', '5', '0'),
11    ('5', '5', '0', '0'),
12    ('5', '5', '5', '0')
13 )
14
15 with open("aoi21x1.test.sp", "w") as f:
16
17     f.write("* AOI21X1 Test\n")
18
19     f.write(".include ../../models/model.t36s.sp\n")
20     f.write(".include ../magic/AOI21X1.spice\n")
21
22     for n in ("a", "b", "c", "y"):
23         f.write(".ic v(%s) = 0\n" % n)
24
25     f.write("V1 vdd gnd 5V\n")
26
27     o_a = ""
28     o_b = ""
29     o_c = ""
30
31     i = 0
32     for state_1, state_2 in itertools.permutations(patterns, 2):
33         # if this state change doesn't change the output, skip it
34         if state_1[-1] == state_2[-1]: continue
35         # if more than one input changed skip it
36         if sum(1 for x, y in zip(state_1[:-1], state_2[:-1]) if x != y) > 1: continue
37         # otherwise execute the state change
38         print(state_1, state_2)
39         for c, a, b, y in (state_1, state_2):
40             o_a += "%dn %sV %fn %sV " % (i*20, a, (i+1)*20-0.00001, a)
41             o_b += "%dn %sV %fn %sV " % (i*20, b, (i+1)*20-0.00001, b)
42             o_c += "%dn %sV %fn %sV " % (i*20, c, (i+1)*20-0.00001, c)
43             i += 1
44
45     print i
46
47     f.write("Va a gnd PWL(%s)\n" % o_a)
48     f.write("Vb b gnd PWL(%s)\n" % o_b)
49     f.write("Vc c gnd PWL(%s)\n" % o_c)
50
51     f.write(".option post\n")
52     f.write(".tran 0.01n %dn\n" % (i*20))
53
54     # measure each crossing
55     for n in range(0, (i/2)):
56         f.write(".meas tran delay_%d when v(y)=2.5 td=%sn cross=1\n" % (n, (n*40)+10))
57
58     f.write(".end\n")

```

Listing 2.6: Python AOI21X1 Spice File Generator

 


Figure 2.16: AOI21X1 Spice Results

State Change	Delay	
0	0.1075n	WORST
1	0.1577n	
2	0.1207n	
3	0.1434n	
4	0.1076n	
5	0.1457n	
6	0.1150n	
7	0.0491n	
8	0.0871n	
9	0.0580n	

Table 2.6: AOI21X1 Delays

2.4.3 MUX2X1 Spice Results

```

1 import itertools
2
3 # S A B Y
4 patterns = (
5     ('0', '0', '0', '5'),
6     ('0', '0', '5', '0'),
7     ('0', '5', '0', '5'),
8     ('0', '5', '5', '0'),
9     ('5', '0', '0', '5'),
10    ('5', '0', '5', '0'),
11    ('5', '5', '0', '0'),
12    ('5', '5', '5', '0')
13 )
14
15 with open("mux2x1_test.sp", "w") as f:
16
17     f.write("* MUX2X1 Test\n")
18
19     f.write(".include ../../models/model.t36s.sp\n")
20     f.write(".include ../magic/MUX2X1.spice\n")
21
22     for n in ("s", "a", "b", "y"):
23         f.write(".ic v(%s) = 0\n" % n)
24
25     f.write("V1 vdd gnd 5V\n")
26
27     o_a = ""
28     o_b = ""
29     o_s = ""
30
31     i = 0
32     for state_1, state_2 in itertools.permutations(patterns, 2):
33         # if this state change doesn't change the output, skip it
34         if state_1[-1] == state_2[-1]: continue
35         # if more than one input changed skip it
36         if sum(1 for x, y in zip(state_1[:-1], state_2[:-1]) if x != y) > 1: continue
37         # otherwise execute the state change
38         print(state_1, state_2)
39         for s, a, b, y in (state_1, state_2):
40             o_s += "%dn %sV %fn %sV " % (i*20, s, (i+1)*20-0.001, s)
41             o_a += "%dn %sV %fn %sV " % (i*20, a, (i+1)*20-0.001, a)
42             o_b += "%dn %sV %fn %sV " % (i*20, b, (i+1)*20-0.001, b)
43             i += 1
44
45     print i
46
47     f.write("Vs s gnd PWL(%s)\n" % o_s)
48     f.write("Va a gnd PWL(%s)\n" % o_a)
49     f.write("Vb b gnd PWL(%s)\n" % o_b)
50
51     f.write(".option post\n")
52     f.write(".tran 0.01n %dn\n" % (i*20))
53
54     # measure each crossing
55     for n in range(0, (i/2)):
56         f.write(".meas tran delay_%d when v(y)=2.5 td=%sn cross=1\n" % (n, (n*40)+10))
57
58     f.write(".end\n")

```

Listing 2.7: Python MUX2X1 Spice File Generator

 


Figure 2.17: MUX2X1 Spice Results

State Change	Delay	
0	0.1536n	
1	0.1342n	
2	0.2569n	
3	0.1542n	
4	0.0832n	
5	0.1340n	
6	0.1390n	
7	0.2571n	WORST
8	0.1391n	
9	0.0788n	
10	0.1464n	
11	0.1467n	

Table 2.7: MUX2X1 Delays

2.4.4 INVX1 Spice Results

```

1 patterns = ("0", "5", "0")
2
3 with open("invx1-test.sp", "w") as f:
4
5     f.write("* INVX1 Test\n")
6
7     f.write(".include ../../models/model.t36s.sp\n")
8     f.write(".include ../magic/INVX1.spice\n")
9
10    for n in ("a", "y"):
11        f.write(".ic v(%s) = 0\n" % n)
12
13    f.write("V1 vdd gnd 5V\n")
14
15    o_a = ""
16
17    for i, d in enumerate(patterns):
18        o_a += "%dn %sV %fn %sV " % (i*20, d, (i+1)*20-0.001, d)
19
20    f.write("Va a gnd PWL(%s)\n" % o_a)
21
22    f.write(".option post\n")
23    f.write(".tran 0.01n %dn\n" % (len(patterns)*20))
24    # measure each crossing
25    f.write(".meas tran delay_0 when v(y)=2.5 td=10n cross=1\n")
26    f.write(".meas tran delay_1 when v(y)=2.5 td=30n cross=1\n")
27    f.write(".end\n")

```

Listing 2.8: Python INVX1 Spice File Generator

 


Figure 2.18: INVX1 Spice Results

State Change	Delay	
0	0.0550n	WORST
1	0.0407n	

Table 2.8: INVX1 Delays

2.4.5 Leaf Component Delay Summary

A table summarizing the worst delays for each gate is shown below.

Component	Worst Delay
AOI21X1	0.1577n
DFFPOSX1	0.4257n
INVX1	0.0550n
MUX2X1	0.2571n

Table 2.9: Worst Case Delay Summary

2.5 VHDL Models With Timing

Using the worst case leaf delays, found above, we updated our VHDL models in order to take the delay into account. All other modules and testbenches required no changes and were left as is.

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity aoi21x1 is
5      generic(delay : time := 0.1577 ns);
6      port(
7          a : in std_logic;
8          b : in std_logic;
9          c : in std_logic;
10         y : out std_logic
11     );
12 end aoi21x1;
13
14 architecture rtl of aoi21x1 is begin
15     process(a, b, c) begin
16         y <= not ((a and b) or c) after delay;
17     end process;
18 end rtl;

```

Listing 2.9: AOI21X1 VHDL Module With Delay

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity dffposx1 is
5      generic(delay : time := 0.4257 ns);
6      port(
7          c : in std_logic;
8          d : in std_logic;
9          q : out std_logic := '0'
10     );
11 end dffposx1;
12
13 architecture rtl of dffposx1 is begin
14     process(c) begin
15         if rising_edge(c) then
16             q <= d after delay;
17         end if;
18     end process;
19 end rtl;

```

Listing 2.10: DFFPOSX1 VHDL Module With Delay

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity invx1 is
5      generic(delay : time := 0.0550 ns);
6      port(
7          a : in std_logic;
8          y : out std_logic
9     );
10 end invx1;
11
12 architecture rtl of invx1 is begin
13     y <= not a after delay;
14 end rtl;

```

Listing 2.11: INVX1 VHDL Module With Delay

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity mux2x1 is
5      generic(delay : time := 0.2571 ns);
6      port(
7          a : in std_logic;
8          b : in std_logic;
9          s : in std_logic;
10         y : out std_logic
11     );
12 end mux2x1;
13
14 architecture rtl of mux2x1 is begin
15     process(a, b, s) begin
16         if (s = '1') then
17             y <= b after delay;
18         else
19             y <= a after delay;
20         end if;
21     end process;
22 end rtl;

```

Listing 2.12: MUX2X1 VHDL Module With Delay

2.6 VHDL Testbench Results With Timing

2.6.1 VHDL Slice Testbench With Delays Waveform

Looking at the outputs of the slice test benches we can see that they perform as expected and match not only the original test benches but the IRSIM and HSpice functional test waveforms. Since we know the delays of each gate and which gates are in each cell there is no need to show a zoomed in waveform illustrating the delay in VHDL, we can simply add up the delays manually as there is no other delay introduced in the simulation.

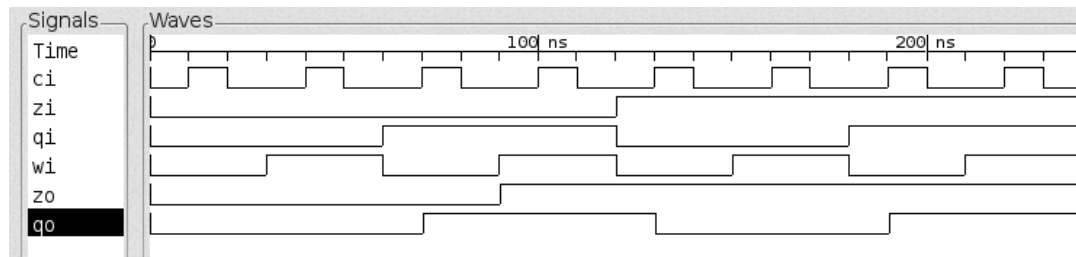


Figure 2.19: VHDL PIN Slice With Delays Waveform

 


Figure 2.20: VHDL Shift Slice With Delays Waveform

2.6.2 VHDL Top Level Testbench With Delays Waveform

Looking at the results of the top level testbenches for both normal and test mode we can see that they are again identical to the waveforms captured without delays. Additionally, since our testbench is exhaustive and self-checking we can be certain that the delays did not introduce any corner cases that one might miss if they are spot checking manually.

 


Figure 2.21: VHDL Top Level Functional Test Bench With Delays Waveform

 


Figure 2.22: VHDL Top Level Test Mode Test Bench With Delays Waveform

2.7 Final Simulation Comparision

Taking a look at the final critical path delay summary we can see that there is a bit of discrepancy between the different simulations. We are not one hundred percent certain why this exists but our best guesses lead to explaining it as an artifact of the different simulation techniques used by each simulator and what parameters they take into account. While there are slight discrepancies all the worst case delays are under 1ns which gives us a theoretical **max clock speed of 1.3GHz**. Since our design is basically all shift registers we should also be able to achieve a throughput equal to the max clock rate. Once we simulate the full layout, which will introduce some long traces between slice rows, we will be able to determine a more accurate maximum clock and throughput rates.

Simulation	PIN	Shift
IRSIM	0.348n	0.242n
SPICE	0.792n	0.455n
VHDL	0.638n	0.682n

Table 2.10: Critical Path Delay Comparison

2.8 Floor Plan

The current floorplan that we plan on pursuing is shown below. From initial placement testing we believe we will be able to achieve a **15x15** grid of slices. The majority of the core functionality is contained in a nice, symmetrically sliced, square. The only additional components that fall outside of this model are the 3 MUXs that are required for test mode. The floor plan shown below indicates the planned location of all test slices and the major components of our design, namely the Shifter and the PIN.

 


Figure 2.23: Floor Plan Diagram

2.9 Major Design Decisions

The major design decisions revolved mainly around the layout of each slice. We knew we wanted to come up with a design that would allow us to tile with minimal effort. Achieving this goal was not necessarily difficult but it required an iterative design process to break out each signal in such a way that would allow them to directly connect together.

Another decision that was made early on was simply ‘which cells should we use?’. While some parts of our slice, such as the D Flip Flop, were obvious choices others were more flexible. In the schematic representation of our PIN slice we show a 2 input AND gate feeding into a 2 input OR gate. As it turns out, the provided library has a cell which performs that function but with an inverted output which is easily mitigated by adding. After comparing two layouts, one using an AND and an OR cell and one using the AOI cell plus an INV cell it turned out that using the AOI and INV saved us some horizontal space which allowed use to fit an extra column of slices in bumping our PIN size to 15x15.

Design decisions revolving around the floor plan are derived from not only from our initial pin layout, which strives to provide chip-to-chip slicing, but also organically as we continue to place components in the frame and see how they fit together. As such, we have not completely finalized the pinout and many pins are still left unassigned. As stated in the first progress report, once we move further into finalizing placement of our Shifter and PIN in the frame we will start tapping off various interesting signals and routing them to close by unassigned pins.

2.10 Work Division

Task	Person
PIN Slice Layout	Thrun
Shift Slice Layout	Qi
PIN Slice IRSIM	Qi
Shift Slice IRSIM	Thrun
PIN Slice Spice	Thrun
Shift Slice Spice	Qi
Gate Spice	Both
VHDL Models	Both
VHDL Slice Tests	Thrun
VHDL Top Tests	Qi
Simulation Comparison	Both
Floor Plan	Both
Design Decisions	Both

Table 2.11: Task Assignment