

# ***INTRANEX***

INTRANEX is a **programmable interconnect network** that accepts a N bit input W and produces a N bit output Z. The interconnect can be programmed to realize any mapping from W to Z.

---

*University of Cincinnati - EECE6080*  
FALL 2013

Max Thrun  
973 919 6593  
max.thrun@gmail.com  
(Coordinator)

Xiaohu Qi  
513 652 2075  
qixiaohuihaha@gmail.com

# Contents

<b>1</b>	<b>Pinout Diagram</b>	<b>4</b>
<b>2</b>	<b>Chip Functionality</b>	<b>6</b>
2.1	Configuring the Programmable Interconnect Network . . . . .	6
2.2	Loading and reading a value . . . . .	6
2.3	Test Mode . . . . .	6
<b>3</b>	<b>Design Decisions</b>	<b>7</b>
<b>4</b>	<b>Block Diagrams</b>	<b>7</b>
4.1	Top Level . . . . .	7
4.2	Parallel Load Shift Register . . . . .	8
4.2.1	Bit-slicing Scheme . . . . .	8
4.2.2	Bit-Slice . . . . .	8
4.3	Programmable Interconnect Network . . . . .	9
4.3.1	Bit-slicing Scheme . . . . .	9
4.3.2	Bit-Slice . . . . .	10
<b>5</b>	<b>VHDL Models</b>	<b>10</b>
5.1	Top Level . . . . .	10
5.2	PIN . . . . .	10
5.3	PIN Slice . . . . .	11
5.4	Shifter . . . . .	12
5.5	Shifter Slice . . . . .	13
5.6	Gates . . . . .	14
<b>6</b>	<b>VHDL Test Benches</b>	<b>16</b>
6.1	Top Level . . . . .	16
6.2	PIN . . . . .	16
6.3	PIN Slice . . . . .	16
6.4	Shifter . . . . .	17
6.5	Shifter Slice . . . . .	17
<b>7</b>	<b>Work Division</b>	<b>19</b>

## List of Figures

1	Pinout Diagram . . . . .	4
2	PIN Configuration . . . . .	6
3	Loading a value . . . . .	6
4	Loading a value and reading the result . . . . .	6
5	Enabling test mode and loading all DFFs . . . . .	6
6	Top Level Block Diagram (3-Bit Configuration) . . . . .	7
7	Parallel Load Bit-Sliced Shifter Register (3-Bit Configuration) . . . . .	8
8	Parallel Load Shifter Register Bit-Slice . . . . .	8
9	Bit-Sliced Programmable Interconnect Network (3-Bit Configuration) . . . . .	9
10	Programmable Interconnect Network Bit-Slice . . . . .	10

## List of Tables

1	Pin Descriptions . . . . .	5
---	----------------------------	---

## Listings

1	PIN VHDL Module . . . . .	10
2	PIN Slice VHDL Module . . . . .	11
3	Parallel Load Shifter VHDL Module . . . . .	12
4	Parallel Load Shifter Slice VHDL Module . . . . .	13
5	AOI21X1 VHDL Module . . . . .	14
6	DFFPOSX1 VHDL Module . . . . .	14
7	INVX1 VHDL Module . . . . .	15
8	MUX2X1 VHDL Module . . . . .	15
9	PIN Slice VHDL Test Bench . . . . .	16
10	Parallel Load Shifter Slice VHDL Test Bench . . . . .	17

# 1 Pinout Diagram

 


Figure 1: Pinout Diagram

Pin #	Name	Type	Description
1	PSI	I	PIN serial input
2	PSO	O	PIN serial output
3	PCLKI	I	PIN clock input
4	PCLKO	O	PIN clock output
5	SI	I	Serial input
6	SO	O	Serial output
7	SCLKI	I	Serial clock input
8	SCLKO	O	Serial clock output
9	LDI	I	Parallel load input (active low)
10	LDO	I	Parallel load output (active low)
11	TII	I	Test inverter input
12	TIO	O	Test interter output
13	TFD	I	Test flip-flop D input
14	TFC	I	Test flip-flop clock input
15	TFQ	O	Test flop-flop Q output
16	TSI	I	Test shift slice serial input
17	TSO	O	Test shift slice serial output
18	TSCI	I	Test shift slice clock input
19	TSCO	O	Test shift slice clock output
20	TSLI	I	Test shift slice load input
21	TSLO	O	Test shift slice load output
22	VDD	P	–
23	GND	P	–
24	–	-	–
25	–	-	–
26	–	-	–
27	–	-	–
28	–	-	–
29	–	-	–
30	–	-	–
31	–	-	–
32	–	-	–
33	–	-	–
34	–	-	–
35	–	-	–
36	–	-	–
37	–	-	–
38	–	-	–
39	–	-	–
40	–	-	–

**Table 1:** Pin Descriptions

## 2 Chip Functionality

### 2.1 Configuring the Programmable Interconnect Network

 


Figure 2: PIN Configuration

### 2.2 Loading and reading a value

 


Figure 3: Loading a value

 


Figure 4: Loading a value and reading the result

### 2.3 Test Mode

 


Figure 5: Enabling test mode and loading all DFFs

### 3 Design Decisions

## 4 Block Diagrams

### 4.1 Top Level

 


Figure 6: Top Level Block Diagram (3-Bit Configuration)

## 4.2 Parallel Load Shift Register

### 4.2.1 Bit-slicing Scheme

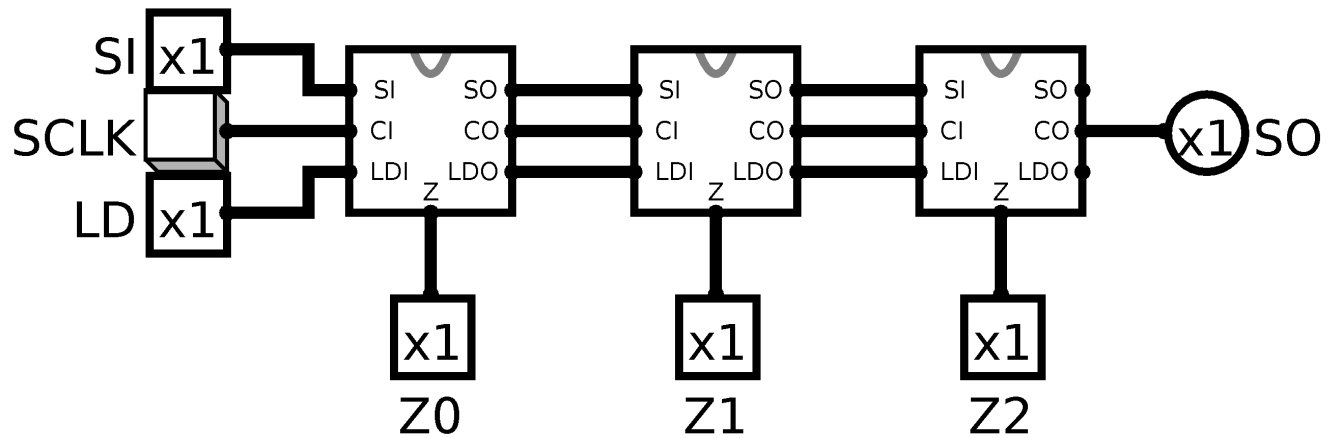


Figure 7: Parallel Load Bit-Sliced Shifter Register (3-Bit Configuration)

### 4.2.2 Bit-Slice


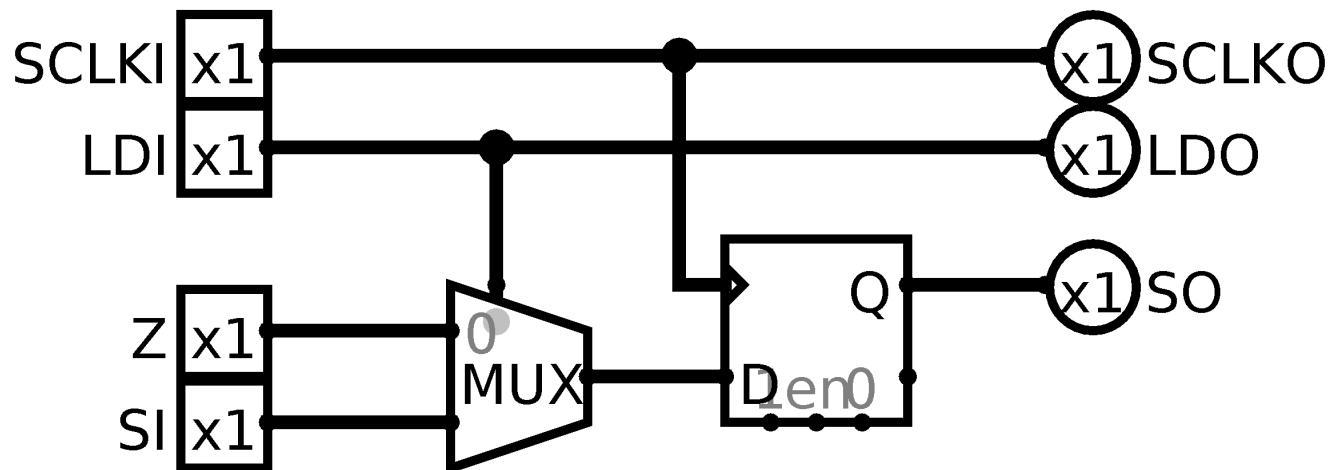


Figure 8: Parallel Load Shifter Register Bit-Slice

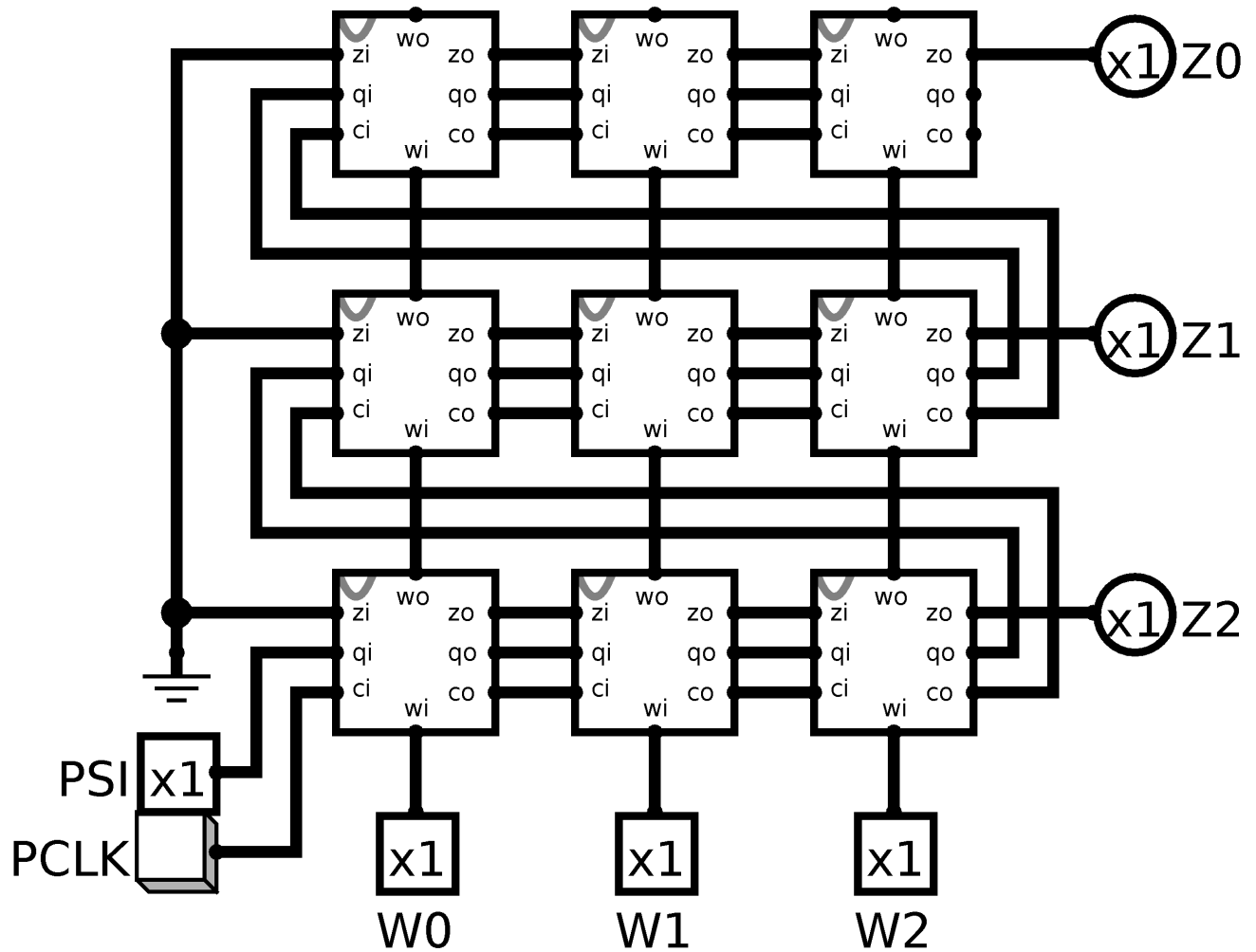

### 4.3 Programmable Interconnect Network

#### 4.3.1 Bit-slicing Scheme



**Figure 9:** Bit-Sliced Programmable Interconnect Network (3-Bit Configuration)

### 4.3.2 Bit-Slice

 


Figure 10: Programmable Interconnect Network Bit-Slice

## 5 VHDL Models

### 5.1 Top Level

### 5.2 PIN

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity pin is
5      generic(
6          n : integer := 3
7      );
8      port(
9          clk : in std_logic;
10         psi : in std_logic;
11         z : out std_logic_vector((n-1) downto 0);
12         w : in std_logic_vector((n-1) downto 0)
13     );
14 end pin;
15
16 architecture rtl of pin is
17
18     component pin_slice is
19         port(
20             zi : in std_logic;
21             qi : in std_logic;
22             wi : in std_logic;
23             ci : in std_logic;
24             zo : out std_logic;
25             qo : out std_logic;

```

```

26         wo : out std_logic;
27         co : out std_logic
28     );
29 end component;
30
31 --type carry_array is array (0 to n) of std_logic_vector(n downto 0);
32 type carry_array is array (0 to n, 0 to n) of std_logic;
33 signal zo : carry_array;
34 signal co : carry_array;
35 signal wo : carry_array;
36 signal qo : carry_array;
37
38 begin
39
40 -- setup first and last inputs for each row
41 z_connect : for i in 0 to n-1 generate
42     zo(i, 0) <= '0';
43     z(i) <= zo(i, n);
44 end generate;
45
46 -- setup first inputs for each column
47 w_connect : for i in 0 to n-1 generate
48     wo(0, i) <= w(i);
49 end generate;
50
51 -- setup row transfer
52 -- (last output of row to first input of next row)
53 r_connect : for i in 0 to n-2 generate
54     qo(i, 0) <= qo(i+1, n);
55     co(i, 0) <= co(i+1, n);
56 end generate;
57
58 -- connect external inputs
59 qo(n-1, 0) <= psi;
60 co(n-1, 0) <= clk;
61
62 -- generate the grid of slices
63 pin_z_gen : for zz in 0 to n-1 generate
64     pin_w_gen : for ww in 0 to n-1 generate
65         pin_i: pin_slice port map(
66             zi => zo(zz, ww),
67             qi => qo(zz, ww),
68             wi => wo(zz, ww),
69             ci => co(zz, ww),
70             zo => zo(zz, ww+1),
71             qo => qo(zz, ww+1),
72             wo => wo(zz+1, ww),
73             co => co(zz, ww+1)
74         );
75     end generate;
76 end generate;
77
78 end rtl;

```

Listing 1: PIN VHDL Module

### 5.3 PIN Slice

---

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity pin_slice is
5      port(
6          zi : in std_logic;
7          qi : in std_logic;
8          wi : in std_logic;
9          ci : in std_logic;
10         zo : out std_logic;
11         qo : out std_logic;
12         wo : out std_logic;
13         co : out std_logic
14     );
15 end pin_slice;
16
17 architecture rtl of pin_slice is
18
19     signal g1_o : std_logic := '0';
20     signal g2_o : std_logic := '0';
21
22 begin
23
24     g1 : entity work.dffposx1 port map(ci, qi, g1_o);
25     g2 : entity work.aoi21x1 port map(wi, g1_o, zi, g2_o);
26     g3 : entity work.invx1 port map(g2_o, zo);
27
28     — pass through
29     co <= ci;
30     wo <= wi;
31     qo <= g1_o;
32
33 end rtl;

```

---

Listing 2: PIN Slice VHDL Module

## 5.4 Shifter

---

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity shift is
5      generic(
6          n : integer := 3
7      );
8      port(
9          clk : in std_logic;
10         ld : in std_logic;
11         si : in std_logic;
12         z : in std_logic_vector((n-1) downto 0);
13         w : out std_logic_vector((n-1) downto 0)
14     );
15 end shift;
16
17 architecture rtl of shift is
18

```

---

```

19     component shift_slice
20     port(
21         sclki : in  std_logic;
22         sclko : out std_logic;
23         ldi   : in  std_logic;
24         ldo   : out std_logic;
25         si    : in  std_logic;
26         so    : out std_logic;
27         z     : in  std_logic
28     );
29     end component;
30
31     -- vector to hold values between slices
32     signal so : std_logic_vector(n downto 0) := (others => '0');
33     signal clko : std_logic_vector(n downto 0) := (others => '0');
34     signal ldo : std_logic_vector(n downto 0) := (others => '0');
35
36     begin
37
38     -- input of slice 0 comes from module input
39     so(0) <= si;
40     ldo(0) <= ld;
41     clko(0) <= clk;
42
43     -- generate N slices
44     shift_gen : for i in 0 to n-1 generate
45         shift_i: shift_slice port map(
46             sclki => clko(i),
47             sclko => clko(i+1),
48             ldi => ldo(i),
49             ldo => ldo(i+1),
50             si => so(i),
51             so => so(i+1),
52             z => z(i)
53         );
54     end generate;
55
56     -- connect the output of each slice to final output vector
57     connect : for i in 0 to n-1 generate
58         w(i) <= so(i+1);
59     end generate;
60
61 end rtl;

```

---

Listing 3: Parallel Load Shifter VHDL Module

## 5.5 Shifter Slice

---

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity shift_slice is
5      port(
6          sclki : in  std_logic;
7          sclko : out std_logic;
8          ldi   : in  std_logic;
9          ldo   : out std_logic;

```

```

10         si      : in  std_logic;
11         so      : out std_logic;
12         z       : in  std_logic
13     );
14 end shift_slice;
15
16 architecture rtl of shift_slice is
17
18     signal g1_o : std_logic := '0';
19
20 begin
21
22     g1 : entity work.mux2x1 port map(z, si, ldi, g1_o);
23     g2 : entity work.dffposx1 port map(sclki, g1_o, so);
24
25     — pass through
26     sclko <= sclki;
27     ldo <= ldi;
28
29 end rtl;

```

---

**Listing 4:** Parallel Load Shifter Slice VHDL Module

## 5.6 Gates

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity aoi21x1 is
5      generic(delay : time := 0 ps);
6      port(
7          a : in std_logic;
8          b : in std_logic;
9          c : in std_logic;
10         y : out std_logic
11     );
12 end aoi21x1;
13
14 architecture rtl of aoi21x1 is begin
15     process(a, b, c) begin
16         y <= not ((a and b) or c) after delay;
17     end process;
18 end rtl;

```

---

**Listing 5:** AOI21X1 VHDL Module

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity dffposx1 is
5      generic(delay : time := 0 ps);
6      port(
7          c : in std_logic;
8          d : in std_logic;
9          q : out std_logic := '0'
10     );

```

```

11 end dffposx1;
12
13 architecture rtl of dffposx1 is begin
14     process(c) begin
15         if rising_edge(c) then
16             q <= d after delay;
17         end if;
18     end process;
19 end rtl;

```

---

**Listing 6:** DFFPOSX1 VHDL Module

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity invx1 is
5     generic(delay : time := 0 ps);
6     port(
7         a : in std_logic;
8         y : out std_logic
9     );
10 end invx1;
11
12 architecture rtl of invx1 is begin
13     y <= not a after delay;
14 end rtl;

```

---

**Listing 7:** INVX1 VHDL Module

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity mux2x1 is
5     generic(delay : time := 0 ps);
6     port(
7         a : in std_logic;
8         b : in std_logic;
9         s : in std_logic;
10        y : out std_logic
11    );
12 end mux2x1;
13
14 architecture rtl of mux2x1 is begin
15     process(a, b, s) begin
16         if (s = '1') then
17             y <= b after delay;
18         else
19             y <= a after delay;
20         end if;
21     end process;
22 end rtl;

```

---

**Listing 8:** MUX2X1 VHDL Module

## 6 VHDL Test Benches

### 6.1 Top Level

### 6.2 PIN

### 6.3 PIN Slice

---

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity pin_slice_tb is
5  end pin_slice_tb;
6
7  architecture tb_rtl of pin_slice_tb is
8
9      signal zi : std_logic := '0';
10     signal qi : std_logic := '0';
11     signal wi : std_logic := '0';
12     signal ci : std_logic := '0';
13     signal zo : std_logic;
14     signal qo : std_logic;
15     signal wo : std_logic;
16     signal co : std_logic;
17
18     component pin_slice
19     port(
20         zi : in std_logic;
21         qi : in std_logic;
22         wi : in std_logic;
23         ci : in std_logic;
24         zo : out std_logic;
25         qo : out std_logic;
26         wo : out std_logic;
27         co : out std_logic;
28     );
29     end component;
30
31 begin
32
33     uut : pin_slice
34     port map(
35         zi => zi,
36         qi => qi,
37         wi => wi,
38         ci => ci,
39         zo => zo,
40         qo => qo,
41         wo => wo,
42         co => co
43     );
44
45     process
46         type pattern_type is record
47             -- inputs
48             zi, qi, wi : std_logic;
49             -- output

```



```

50         zo : std_logic;
51     end record;
52
53     type pattern_array is array (natural range <>) of pattern_type;
54     constant patterns : pattern_array :=
55         — zi   qi   wi   zo
56         (('0','0','0','0'),
57          ('0','0','1','0'),
58          ('0','1','0','0'),
59          ('0','1','1','1'),
60          ('1','0','0','1'),
61          ('1','0','1','1'),
62          ('1','1','0','1'),
63          ('1','1','1','1'));
64
65     begin
66         — check each pattern
67         for i in patterns'range loop
68
69             — set the inputs
70             zi <= patterns(i).zi;
71             qi <= patterns(i).qi;
72             wi <= patterns(i).wi;
73             wait for 10 ns;
74
75             — pulse the clock and check clock passthrough
76             ci <= '1';
77             wait for 10 ns;
78             assert co = '1' report "CO does not equal 1" severity error;
79             ci <= '0';
80             wait for 10 ns;
81             assert co = '0' report "CO does not equal 0" severity error;
82
83             — check the outputs
84             assert qo = patterns(i).qi report "QI not equal QO" severity error;
85             assert zo = patterns(i).zo report "ZO does not match pattern" severity error;
86
87         end loop;
88
89         report "Test Complete" severity note;
90         wait;
91
92     end process;
93
94 end tb_rtl;

```

Listing 9: PIN Slice VHDL Test Bench

## 6.4 Shifter

## 6.5 Shifter Slice

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity shift_slice_tb is

```

```

5  end shift_slice_tb;
6
7  architecture tb_rtl of shift_slice_tb is
8
9      signal sclki : std_logic := '0';
10     signal sclko : std_logic;
11     signal ldi   : std_logic := '0';
12     signal ldo   : std_logic;
13     signal si    : std_logic := '0';
14     signal so    : std_logic;
15     signal z     : std_logic := '0';
16
17     component shift_slice is
18     port(
19         sclki : in  std_logic;
20         sclko : out std_logic;
21         ldi   : in  std_logic;
22         ldo   : out std_logic;
23         si    : in  std_logic;
24         so    : out std_logic;
25         z     : in  std_logic
26     );
27     end component;
28
29 begin
30
31     uut : shift_slice
32     port map(
33         sclki => sclki ,
34         sclko => sclko ,
35         ldi   => ldi   ,
36         ldo   => ldo   ,
37         si    => si    ,
38         so    => so    ,
39         z     => z
40     );
41
42     process
43         type pattern_type is record
44             -- inputs
45             ldi, z, si : std_logic;
46             -- output
47             so : std_logic;
48         end record;
49
50         type pattern_array is array (natural range <>) of pattern_type;
51         constant patterns : pattern_array :=
52             -- ldi  z  si  so
53             (( '0', '0', '0', '0'),
54              ('0', '0', '1', '0'),
55              ('0', '1', '0', '1'),
56              ('0', '1', '1', '1'),
57              ('1', '0', '0', '0'),
58              ('1', '0', '1', '1'),
59              ('1', '1', '0', '0'),
60              ('1', '1', '1', '1'));
61
62     begin
63         -- check each pattern

```

```

64     for i in patterns 'range loop
65
66         — set the inputs
67         ldi <= patterns(i).ldi;
68         z  <= patterns(i).z;
69         si <= patterns(i).si;
70         wait for 10 ns;
71
72         — pulse the clock and check clock passthrough
73         sclki <= '1';
74         wait for 10 ns;
75         assert sclko = '1' report "SCLKO does not equal 1" severity error;
76         assert ldo = patterns(i).ldi report "SCLKO does not equal 1" severity error;
77         sclki <= '0';
78         wait for 10 ns;
79         assert sclko = '0' report "SCLKO does not equal 0" severity error;
80         assert ldo = patterns(i).ldi report "SCLKO does not equal 1" severity error;
81
82         — check the output
83         assert so = patterns(i).so report "SO is incorrect" severity error;
84
85     end loop;
86
87     report "Test Complete" severity note;
88     wait;
89
90 end process;
91
92 end tb_rtl;

```

---

Listing 10: Parallel Load Shifter Slice VHDL Test Bench

## 7 Work Division